

Capacitors DPP Solutions Level 2



30 July 2020

02:30

Q1:→

here are 3 capacitors

2 of Dielect. filled
1 is air capacitor

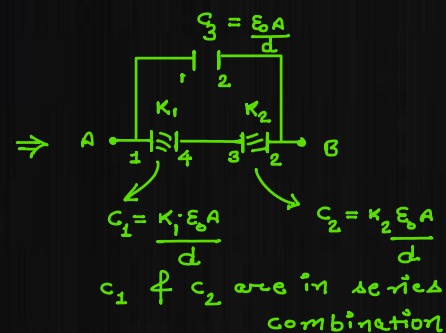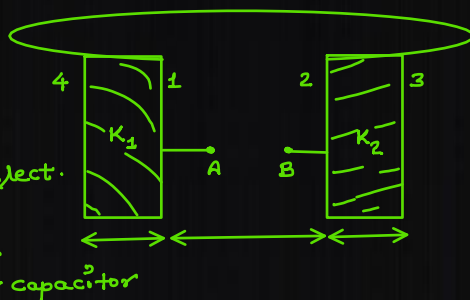


$$\therefore C_{12} = \frac{C_1 \cdot C_2}{C_1 + C_2} = \frac{K_1 K_2 \epsilon_0 A}{(K_1 + K_2)} F$$

C_{12} & C_3 are in parallel ;

$$\begin{aligned} \therefore C_{eq} &= C_{12} + C_3 \\ &= \frac{K_1 K_2 \epsilon_0 A}{(K_1 + K_2)} + \frac{\epsilon_0 A}{d} \\ C_{eq} &= \frac{(K_1 K_2 + K_1 + K_2) \cdot \epsilon_0 A}{(K_1 + K_2) \cdot d} \end{aligned}$$


Q2:→

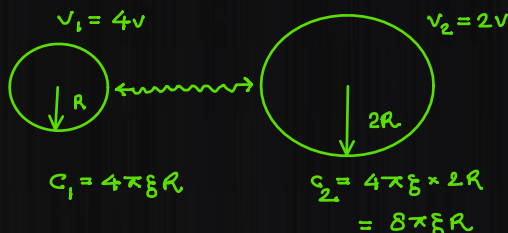

\therefore loss in Energy due to redistribution

$$\begin{aligned} \Delta U &= \frac{C_1 \cdot C_2 \cdot (V_1 - V_2)^2}{2(C_1 + C_2)} \\ &= \frac{4\pi\epsilon R \times 8\pi\epsilon R \times (4V - 2V)^2}{2 \times 12\pi\epsilon R} \\ &= \frac{4}{3} \pi\epsilon R \times 4V^2 \\ \therefore \Delta U &= \frac{16\pi\epsilon R V^2}{3} \text{ Joules} \end{aligned}$$

Q3)

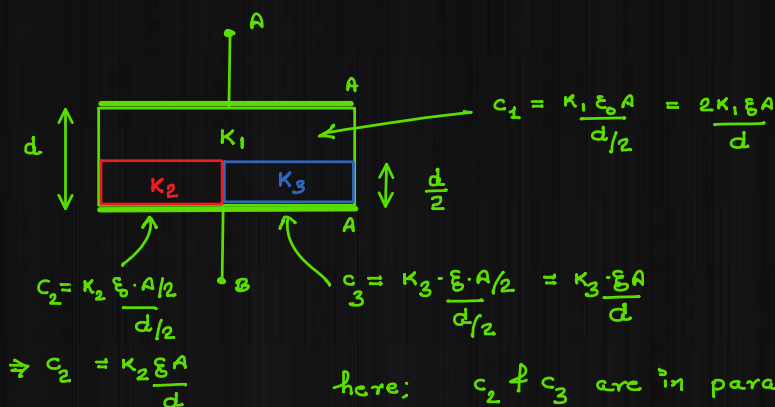

here; C_2 & C_3 are in parallel ;

$$\begin{aligned} \therefore C_{23} &= C_2 + C_3 \\ \Rightarrow C_{23} &= (K_2 + K_3) \cdot \frac{\epsilon_0 A}{d} \quad \text{--- (1)} \end{aligned}$$


C_1 & C_{23} are in series ;

$$\begin{aligned} C_{eq} &= \frac{C_1 \cdot C_{23}}{C_1 + C_{23}} = \frac{2K_1 \frac{\epsilon_0 A}{d} \times (K_2 + K_3) \frac{\epsilon_0 A}{d}}{\{2K_1 + (K_2 + K_3)\} \cdot \frac{\epsilon_0 A}{d}} \\ \therefore C_{eq} &= \frac{2K_1 \cdot (K_2 + K_3) \cdot \epsilon_0 A}{\{2K_1 + (K_2 + K_3)\} \cdot d} \end{aligned}$$

Q4:



Q4.

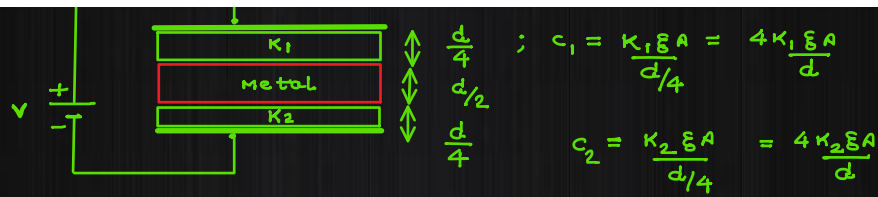

presence of metal decreases the electric field b/w the plates.

$\therefore C_1$ & C_2 are in series

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{4K_1 \frac{\epsilon_0 A}{d} \times 4K_2 \frac{\epsilon_0 A}{d}}{4K_1 \frac{\epsilon_0 A}{d} + 4K_2 \frac{\epsilon_0 A}{d}} = \frac{4 \cdot \epsilon_0 A (K_1 + K_2)}{d}$$

$$\Rightarrow C_{eq} = \frac{4K_1 K_2 \cdot \epsilon_0 A}{(K_1 + K_2) \cdot d}$$

so initial energy of the system (U_i) = $\frac{1}{2} C_{eq} \cdot V^2$

$$\Rightarrow U_i = \frac{2K_1 K_2 \epsilon_0 A \cdot V^2}{(K_1 + K_2) \cdot d} \quad \text{--- (1)}$$

on removing the metal plate, air fills in the space

$$C_{air} = \frac{\epsilon_0 A}{d/2} = \frac{2\epsilon_0 A}{d}$$

as C_1 , C_{air} & C_2 comes in series

$$\frac{1}{C_{eq}'} = \frac{1}{C_1} + \frac{1}{C_{air}} + \frac{1}{C_2}$$

$$\Rightarrow \frac{1}{C_{eq}'} = \frac{d}{4K_1 \epsilon_0 A} + \frac{d}{2\epsilon_0 A} + \frac{d}{4K_2 \epsilon_0 A}$$

$$= \frac{d}{2\epsilon_0 A} \cdot \left\{ \frac{1}{2K_1} + 1 + \frac{1}{2K_2} \right\}$$

$$\Rightarrow \frac{1}{C_{eq}'} = \frac{d}{4K_1 K_2 \epsilon_0 A} \cdot \{2K_1 K_2 + K_1 + K_2\}$$

$$\Rightarrow C_{eq}' = \frac{4K_1 K_2 \epsilon_0 A}{(2K_1 K_2 + K_1 + K_2) \cdot d}$$

so final energy of the system (U_f) = $\frac{1}{2} C_{eq}' \cdot V^2$

$$\Rightarrow U_f = \frac{2K_1 K_2 \epsilon_0 A \cdot V^2}{d \cdot (2K_1 K_2 + K_1 + K_2)}$$



so work done in removing the metal slab.



$$W = \Delta U = U_f - U_i$$

$$= \frac{2K_1 K_2 \epsilon_0 A V^2}{d} \cdot \left[\frac{1}{(2K_1 K_2 + K_1 + K_2)(K_1 + K_2)} - \frac{1}{(K_1 + K_2)} \right]$$

$$\Rightarrow W = \frac{-4K_1 K_2^2 \epsilon_0 A V^2}{(K_1 + K_2) \cdot (2K_1 K_2 + K_1 + K_2)} \quad \text{Joule.}$$

Q5)

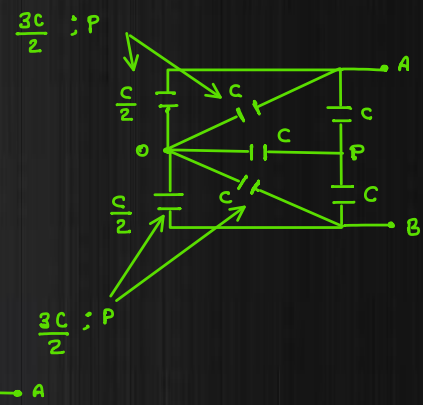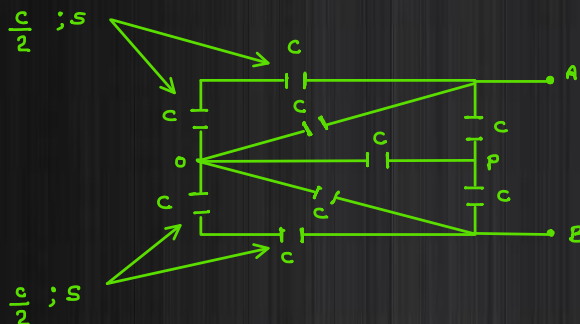

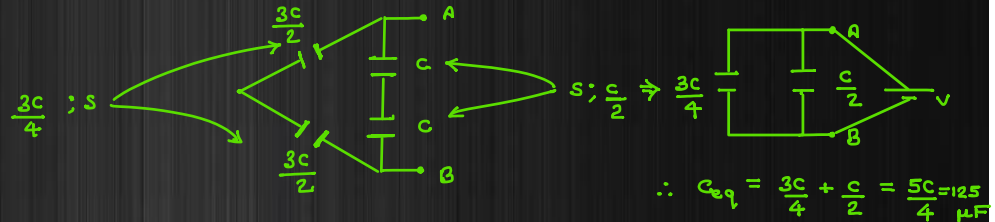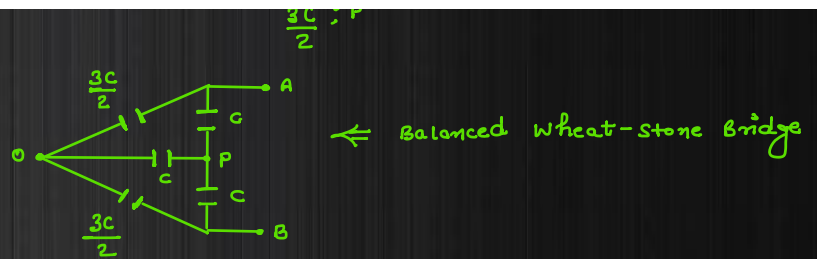


$$\therefore U = \frac{1}{2} C_{eq} \cdot V^2$$

$$= \frac{1}{2} \times 125 \times 10^{-6} \times 12^2$$

Energy of the system $\therefore U = 9000 \mu J$

Q6:→

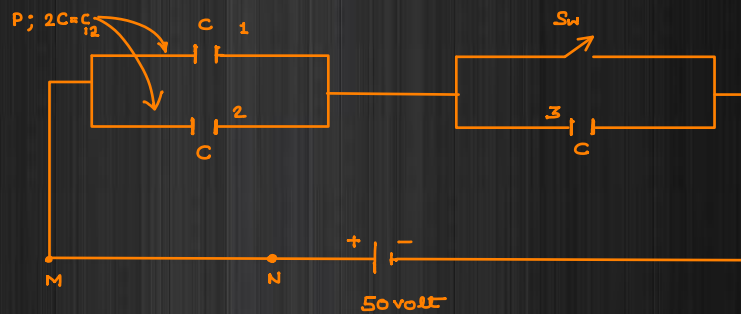

Before closing the switch;

C_{12} & C_3 are in series

$$C_{eq} = \frac{C_{12} \times C_3}{C_{12} + C_3} = \frac{2C \times C}{2C + C} = \frac{2C}{3} \text{ --- (1)}$$

initial charge flown from the battery

$$q_1 = C_{eq} \cdot V = \frac{2CV}{3} \text{ --- (2)}$$

as we close the switch C_3 becomes short circuited.

so no charge will store in C_3

\therefore new equivalent capacitance

$$C_{eq}' = 2C \text{ --- (3)}$$

so new charge flown from the battery

$$q' = C_{eq}' \cdot V = 2CV \text{ --- (4)}$$

so extra charge flown from the battery

$$\Delta q = q' - q = 2CV - \frac{2CV}{3}$$


$$\Rightarrow \Delta q = \frac{4CV}{3} \text{ --- (5)}$$


$$\therefore \Delta q_{MN} = \frac{4CV}{3} = \frac{4}{3} \times 5 \times 10^{-6} \times 50$$

$$= \frac{1000}{3} \times 10^{-6} C$$

$$\therefore \Delta q_{MN} = 333.3 \mu C$$

Q7)

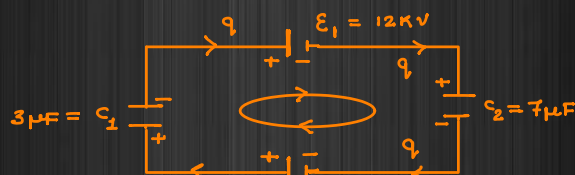

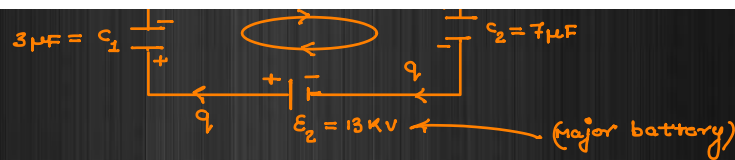

applying KVL in the close loop;


$$-\varepsilon_1 - \frac{q}{C_2} + \varepsilon_2 - \frac{q}{C_1} = 0$$

$$\Rightarrow q \cdot (C_1 + C_2) = (\varepsilon_2 - \varepsilon_1)$$

$$P.D. \text{ across } C_1 \left(\frac{q}{C_1} \right) = \frac{C_2 \cdot (\varepsilon_2 - \varepsilon_1)}{(C_1 + C_2)} = \frac{7 \times 10^{-6} \times 10^3}{10 \times 10^{-6}} = 700 \text{ volt}$$

$$P.D. \text{ across } C_2 \left(\frac{q}{C_2} \right) = \frac{C_1 \cdot (\varepsilon_2 - \varepsilon_1)}{(C_1 + C_2)} = \frac{3 \times 10^{-6} \times 10^3}{10 \times 10^{-6}} = 300 \text{ volt}$$

Q8) :->

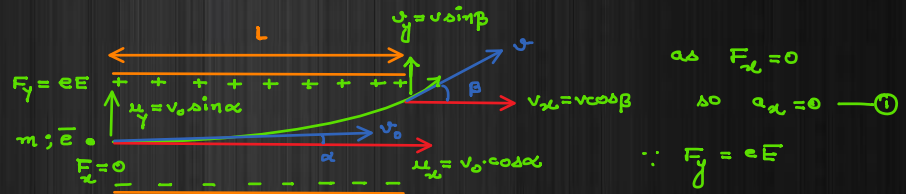

along x-axis

$$\vec{u}_x = \vec{u}_{x0} + \vec{a}_x \cdot t$$

$$u \cos \beta = u_0 \cos \alpha + 0 \cdot t$$

$$\Rightarrow u = \frac{u_0 \cdot \cos \alpha}{\cos \beta} \quad (3)$$

so Kinetic Energy at the moment e comes out:

$$K = \frac{1}{2} m u^2$$

$$\therefore K = \frac{m \cdot u_0^2 \cdot \cos^2 \alpha}{2 \cdot \cos^2 \beta} \quad (4)$$

$$\therefore s_x = u_{x0} \cdot t + \frac{1}{2} a_{x0} \cdot t^2$$

$$\therefore L = u_0 \cdot \cos \alpha \cdot t + \frac{1}{2} \cdot 0 \cdot t^2$$

$$\therefore t = \frac{L}{u_0 \cos \alpha} \quad (5) \quad ; \quad \text{time taken by the } e \text{ to come out of the plates}$$

along y-axis

$$\vec{u}_y = \vec{u}_{y0} + \vec{a}_y \cdot t$$

$$u \sin \beta = u_0 \sin \alpha + \frac{eE}{m} \cdot \frac{L}{u_0 \cos \alpha}$$

$$\Rightarrow \frac{u_0 \cdot \cos \alpha \cdot \sin \beta}{\cos \beta} = u_0 \sin \alpha + \frac{eEL}{m u_0 \cos \alpha}$$


$$\Rightarrow u_0 \cdot \{ \cos \alpha \tan \beta - \sin \alpha \} = \frac{eEL}{m u_0 \cos \alpha}$$

$$\Rightarrow u_0 \cdot \cos \alpha \cdot \{ \tan \beta - \tan \alpha \} = \frac{eEL}{m u_0 \cos \alpha}$$

$$\therefore E = \frac{m u_0^2 \cdot \cos^2 \alpha (\tan \beta - \tan \alpha)}{eL}$$

Q10) :->



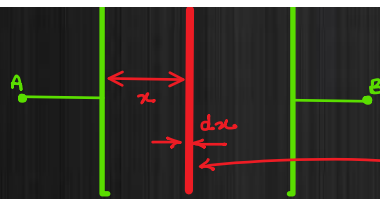


$$dC = \frac{\kappa x \cdot \epsilon_0 A}{dx} = (\kappa_0 + \alpha x) \cdot \epsilon_0 \cdot \frac{a^2}{d} \quad (\text{capacitance of the elementary strip})$$

as all such elements lies in series

$$\begin{aligned} \therefore \frac{1}{C_{eq}} &= \int \frac{1}{dC} \\ &= \int_0^d \frac{dx}{(\kappa_0 + \alpha x) \cdot a^2 \cdot \epsilon_0} \\ &= \frac{1}{\epsilon_0 \cdot a^2} \cdot \left\{ \frac{1}{\alpha} \cdot \log_e (\kappa_0 + \alpha x) \right\}_0^d \\ &= \frac{1}{\epsilon_0 \cdot \alpha \cdot a^2} \cdot \left\{ \log_e (\kappa_0 + \alpha \cdot d) - \log_e (\kappa_0) \right\} \\ &= \frac{1}{\epsilon_0 \cdot \alpha \cdot a^2} \cdot \left\{ \log_e \left(\frac{\kappa_0 + \alpha d}{\kappa_0} \right) \right\} \\ \therefore C_{eq} &= \frac{\epsilon_0 \cdot \alpha \cdot a^2}{\log_e \left(1 + \frac{\alpha d}{\kappa_0} \right)} \end{aligned}$$

Q9: → a)

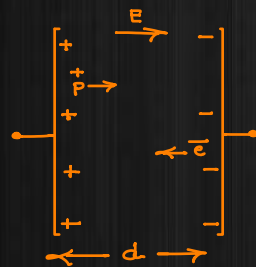

$$\text{acceleration of } \bar{e} (a_e) = \frac{eE}{m_e}$$

$$" " p (a_p) = \frac{eE}{m_p}$$

i) if velocity of projection is same i.e. $u_e = u_p = u$ (let)


$$\text{from: } \vec{s} = \vec{u}t + \frac{1}{2}\vec{a} \cdot t^2$$

$$d = u \cdot t_e + \frac{eE}{m_e} \cdot t_e^2 \quad \text{--- (1)} \quad d = u \cdot t_p + \frac{1}{2} \cdot \frac{eE}{m_p} \cdot t_p^2 \quad \text{--- (2)}$$

comparing (1) & (2)

$$t_e < t_p$$

b)

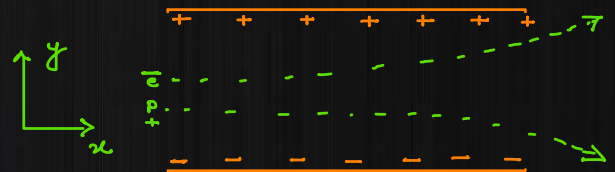

for a charge particle of mass 'm' & charge 'q'.

$$\text{from: } v_x = u_x + a_x \cdot t$$

$$v \cos \theta = u + 0$$

$$\text{final speed } \therefore v = \frac{u}{\cos \theta} \quad \text{--- (1)}$$

$$\therefore s_x = u_x \cdot t + \frac{1}{2} a_x \cdot t^2$$

$$L = u \cdot t + 0$$

$$\text{time taken } \therefore t = \frac{L}{u} \quad \text{--- (2)}$$

to come out

of the plates

$$\text{from: } \vec{v}_y = \vec{u}_y + \vec{a}_y \cdot t$$

$$\Rightarrow v \sin \theta = 0 + \frac{qE}{m} \cdot t$$

$$\text{from (2) \& (3)} \Rightarrow u \cdot \tan \theta = \frac{qE}{m} \cdot \frac{L}{u}$$

$$\text{angle of deviation} \Rightarrow \theta = \tan^{-1} \left\{ \frac{qEL}{mu} \right\} \quad \text{--- (*)}$$

$$\text{or } \tan^{-1} \left\{ \frac{qEL}{P} \right\}$$

$$\text{or } \tan^{-1} \left\{ \frac{qEL}{\sqrt{2Km}} \right\}$$

i) if initial speed is same;

$$u_e = u_p = u ; q_e = q_p = e ; m_p > m_e$$

$$\therefore \boxed{\theta_p < \theta_e}$$

ii) for same initial K.E. ;

$$K_e = K_p = K ; q_e = q_p = e ; m_p > m_e$$

$$\text{again : } \boxed{\theta_p < \theta_e}$$

iii) for same initial momentum ;

$$p_e = p_p = P ; q_e = q_p = e$$

$$\therefore \boxed{\theta_p = \theta_e}$$