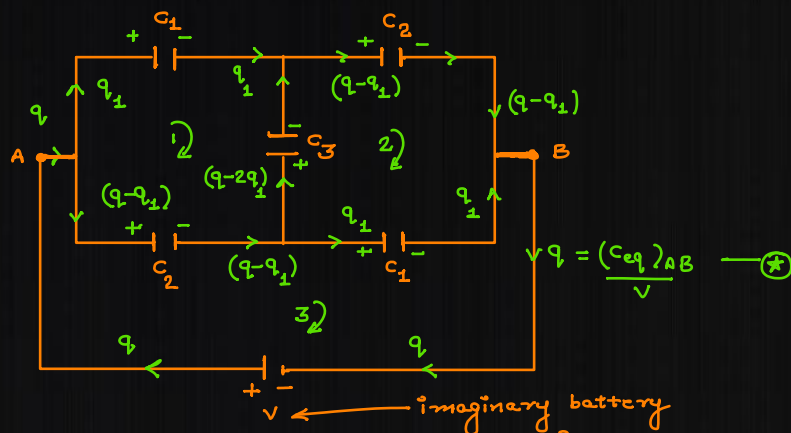


capacitor circuits

25 July 2020 11:16

Q: find the equivalent capacitance b/w points A & B.



Reverse symmetry Problem \rightarrow In this case identical capacitors are connected diagonally opposite to a wheat-stone bridge, the identical capacitors carry same charge and the potential difference b/w their plates will be same.

applying KVL in loop 1 \rightarrow

$$-\frac{q_1}{C_1} + \frac{(q-2q_1)}{C_3} + \frac{(q-q_1)}{C_2} = 0 \quad \text{--- (1)}$$

applying KVL in loop 3 \rightarrow

$$-(q-q_1) - \frac{q_1}{C_1} + V = 0 \quad \text{--- (2)}$$

eqn (1) + (2)

$$-2q_1 + \frac{(q-2q_1)}{C_3} + V = 0$$

$$\Rightarrow 2q_1 \cdot \left\{ \frac{1}{C_1} + \frac{1}{C_3} \right\} = V + \frac{q}{C_3}$$

$$\therefore 2q_1 \cdot \left\{ \frac{C_1 + C_3}{C_1 C_3} \right\} = \left(\frac{C_3 V + q}{C_3} \right)$$

$$\Rightarrow q_1 = \frac{C_1 \cdot (C_3 V + q)}{2(C_1 + C_3)} \quad \text{--- (3)}$$

from (1) & (2)

$$C_1 \cdot \frac{(C_3 V + q)}{2(C_1 + C_3)} = \frac{(C_2 V - q) \cdot C_1}{(C_2 - C_1)}$$

$$\Rightarrow q \cdot \left\{ \frac{1}{2(C_1 + C_3)} + \frac{1}{(C_2 - C_1)} \right\} = V \cdot \left\{ \frac{C_2}{(C_2 - C_1)} - \frac{C_3}{2(C_1 + C_3)} \right\}$$

$$\Rightarrow q \cdot \{ C_2 - C_1 + 2C_1 + 2C_3 \} = V \{ 2C_1 C_2 + 2C_2 C_3 - C_2 C_3 + C_3^2 \}$$

$$\frac{q}{V} = \frac{(2C_1 C_2 + C_2 C_3 + C_1 C_3)}{(C_1 + C_2 + 2C_3)}$$

$$\therefore C_{eq} = \frac{q}{V} = \frac{2C_1 C_2 + C_3 (C_1 + C_2)}{(C_1 + C_2 + 2C_3)} =$$

Q: what amount of heat will appear in the circuit if the key is shifted from position 1 to 2.

Q: What amount of heat will appear in the circuit if the key is shifted from position 1 to 2.

Solution \rightarrow

There are two ways by which heat appears in any circuit


i) Loss in Energy of capacitor system

$$\text{ie; } H_{\text{cap}} = \Delta U_{\text{cap}} = (U_f - U_i)$$

if $U_f < U_i$

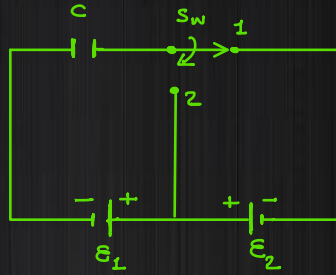
ii) Heat appeared in the cells

$$H_{\text{cell}} = \frac{W_{\text{Batt}}}{2} = \frac{\Delta q \times V_{\text{Batt}}}{2}$$



Case 1 \rightarrow

when the switch was at position 1

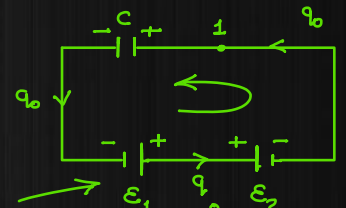

major Battery

from KVL

$$\varepsilon_1 - \varepsilon_2 - \frac{q_0}{C} = 0$$


$$\text{so } q_0 = C \cdot (\varepsilon_1 - \varepsilon_2)$$

initial charge on the capacitor — (1)

$$\text{so initial Energy stored } \Rightarrow U_i = \frac{1}{2} \cdot \frac{q_0^2}{C} = \frac{C(\varepsilon_1 - \varepsilon_2)^2}{2} \quad \text{--- (2)}$$

after shifting the key at position 2

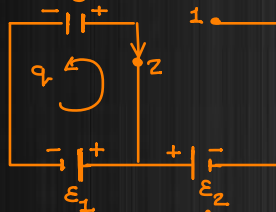Battery 2 becomes open circuit (Disconnected)
if 'c' comes directly in parallel with ε_1



so no charge will flow from ε_2

$$\text{ie; } q_2' = 0 \quad \text{--- (3)}$$

so the final charge on 'c'

$$q = C\varepsilon_1 \quad \text{--- (4)}$$

$$\therefore \text{final Energy stored } (U_f) = \frac{1}{2} \frac{q^2}{C} = \frac{1}{2} C\varepsilon_1^2 \quad \text{--- (5)}$$

$$\text{as } U_f > U_i$$

so no heat will appear in the capacitor.

$$\text{Now, heat appeared in the cell 1 } (H_1) = \frac{W_1}{2} = \frac{\Delta q_1 \cdot \varepsilon_1}{2} = \frac{(q - q_0) \cdot \varepsilon_1}{2} = \left\{ C\varepsilon_1 - C(\varepsilon_1 - \varepsilon_2) \right\} \cdot \frac{\varepsilon_1}{2}$$

$$\Rightarrow H_1 = \frac{C\varepsilon_1\varepsilon_2}{2} \quad \text{--- (6)}$$

$$\text{if heat appeared in the cell 2 } (H_2) = \frac{W_2}{2} = \frac{\Delta q_2 \cdot \varepsilon_2}{2} = \frac{(q' - q_0) \cdot \varepsilon_2}{2}$$

$$= \left\{ 0 - C(\varepsilon_1 - \varepsilon_2) \right\} \cdot \frac{\varepsilon_2}{2}$$


$$\therefore H_2 = \left(\frac{C\varepsilon_2^2}{2} - C\varepsilon_1\varepsilon_2 \right) \quad \text{--- (7)}$$


\therefore Total heat generated

$$H_{\text{total}} = H_1 + H_2 = \frac{C\varepsilon_1\varepsilon_2}{2} + \left(\frac{C\varepsilon_2^2}{2} - C\varepsilon_1\varepsilon_2 \right)$$

$$H_{\text{total}} = \frac{C\varepsilon_2^2}{2} \text{ Joule}$$

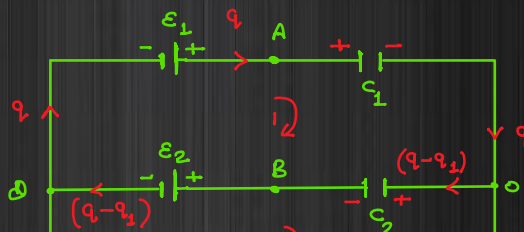Q: \rightarrow find the P.D. b/w points A & O.



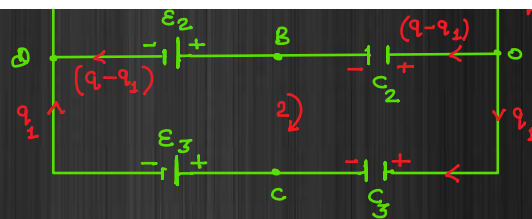

← applying KVL in loop 1: →

$$\varepsilon_1 - \frac{q}{C_1} - \frac{(q - q_1)}{C_2} - \varepsilon_2 = 0$$

$$\Rightarrow \frac{q_1}{C_2} - q \cdot \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = (\varepsilon_2 - \varepsilon_1)$$

$$\Rightarrow \frac{q_1}{C_2} = (\varepsilon_2 - \varepsilon_1) + q \cdot \left(\frac{C_1 + C_2}{C_1 C_2} \right) \quad \text{--- ①}$$

$$\Rightarrow q_1 = \frac{C_1 C_2 (\varepsilon_2 - \varepsilon_1) + q (C_1 + C_2)}{C_1}$$

← applying KVL in loop 2: →

$$\varepsilon_2 + \frac{(q - q_1)}{C_2} - \frac{q_1}{C_3} - \varepsilon_3 = 0$$

$$\Rightarrow \frac{q}{C_2} - q_1 \cdot \left(\frac{1}{C_2} + \frac{1}{C_3} \right) = (\varepsilon_3 - \varepsilon_2)$$

$$\Rightarrow \frac{q}{C_2} - q_1 \cdot \left(\frac{C_2 + C_3}{C_2 C_3} \right) = (\varepsilon_3 - \varepsilon_2)$$

$$\Rightarrow q_1 \cdot \left(\frac{C_2 + C_3}{C_2 C_3} \right) = (\varepsilon_2 - \varepsilon_3) + \frac{q}{C_2}$$

$$\Rightarrow q_1 \cdot \left(\frac{C_2 + C_3}{C_3} \right) = \frac{C_2 (\varepsilon_2 - \varepsilon_3) + q}{C_2}$$

$$q_1 = \frac{C_3 \cdot \{ C_2 (\varepsilon_2 - \varepsilon_3) + q \}}{(C_2 + C_3)} \quad \text{--- ②}$$

from ① & ②

$$C_3 \cdot \left\{ \frac{C_2 (\varepsilon_2 - \varepsilon_3) + q}{(C_2 + C_3)} \right\} = \left\{ \frac{C_1 C_2 (\varepsilon_2 - \varepsilon_1) + q (C_1 + C_2)}{C_1} \right\}$$

$$\Rightarrow \frac{C_2 C_3 (\varepsilon_2 - \varepsilon_3) - C_1 C_2 (\varepsilon_2 - \varepsilon_1)}{(C_2 + C_3)} = q \cdot \left[\frac{(C_1 + C_2)}{C_1} - \frac{C_3}{(C_2 + C_3)} \right]$$


$$\Rightarrow C_1 C_2 C_3 \varepsilon_2 - C_1 C_2 C_3 \varepsilon_3 - (C_1 C_2^2 + C_1 C_2 C_3) (\varepsilon_2 - \varepsilon_1) = q [C_1 C_2 + C_1 C_3 + C_2^2 + C_2 C_3 - C_1 C_3]$$


$$\Rightarrow (C_1 C_2 C_3 \varepsilon_2 - C_1 C_2 C_3 \varepsilon_3 - C_1 C_2^2 \varepsilon_2 - C_1 C_2 C_3 \varepsilon_2 + C_1 C_2^2 \varepsilon_1 + C_1 C_2 C_3 \varepsilon_1) = q \cdot (C_1 C_2 + C_2^2 + C_2 C_3)$$

$$\Rightarrow C_1 C_2 (-C_3 \varepsilon_3 - C_2 \varepsilon_2 + C_2 \varepsilon_1 + C_3 \varepsilon_1) = q \cdot C_2 (C_1 + C_2 + C_3)$$

potential diff. b/w points A & O. $\Rightarrow \frac{q}{C_1} = \frac{\varepsilon_1 (C_2 + C_3) - C_2 \varepsilon_2 - C_3 \varepsilon_3}{(C_1 + C_2 + C_3)} = \Delta V_{AB}$

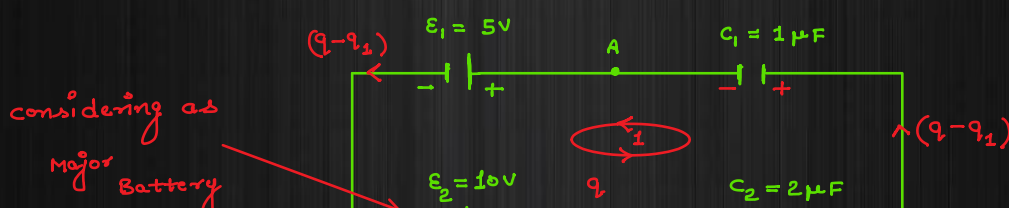Q; in the above question if $C_1 = 1 \mu F$, $C_2 = 2 \mu F$, $C_3 = 3 \mu F$ & $\varepsilon_1 = 5V$, $\varepsilon_2 = 10V$ & $\varepsilon_3 = 5V$ volt. Find the P.D b/w i) A & B ii) A & C iii) B & C iv) D & O



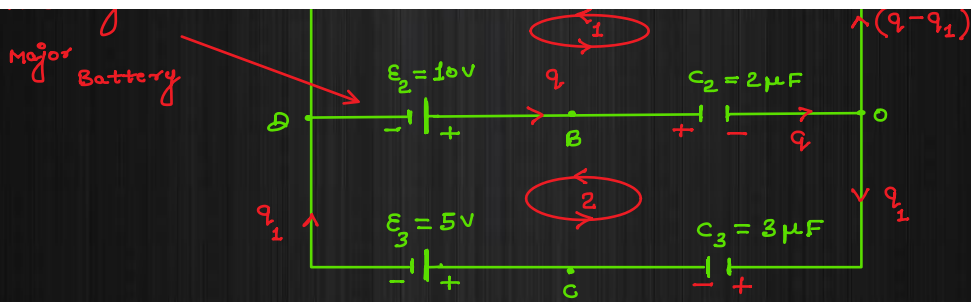

$$\begin{aligned} \text{KVL in loop 1} \Rightarrow 10 - \frac{q}{2} - \frac{(q - q_1)}{1} - 5 &= 0 \\ \Rightarrow 5 - \frac{3q}{2} + q_1 &= 0 \\ \Rightarrow \frac{3q}{2} - q_1 &= 5 \\ \Rightarrow 3q - 2q_1 &= 10 \quad \text{--- (1)} \end{aligned}$$

$$\begin{aligned} \text{KVL in loop 2} \Rightarrow 5 + \frac{q_1}{3} + \frac{q}{2} - 10 &= 0 \\ \Rightarrow \frac{q}{2} + \frac{q_1}{3} &= 5 \\ \Rightarrow 3q + 2q_1 &= 30 \quad \text{--- (2)} \end{aligned}$$

$$\begin{aligned} \text{eqn (1) + (2)} \\ 6q &= 40 \\ \Rightarrow q &= \frac{20}{3} \mu\text{C} \quad \text{--- (3)} \end{aligned}$$

$$\begin{aligned} \text{from (1)} \\ 3 \times \frac{20}{3} - 2q_1 &= 10 \\ \Rightarrow 20 - 2q_1 &= 10 \\ \Rightarrow q_1 &= \frac{10}{2} = 5 \mu\text{C} \quad \text{--- (4)} \end{aligned}$$

$$\text{so } (q - q_1) = \frac{20}{3} - 5 = \frac{5}{3} \mu\text{C} \quad \text{--- (5)}$$

$$\begin{aligned} \star) \text{ P.D. b/w } A \text{ \& } B \text{ } (\Delta V_{AB}) &= (V_A - V_B) = (V_A - V_0) + (V_0 - V_B) \\ &= \left\{ -\frac{(q - q_1)}{C_1} \right\} + \left\{ -\frac{q}{C_2} \right\} \\ &= -\frac{5}{3 \times 1} - \frac{20}{3 \times 2} \\ \therefore \Delta V_{AB} &= -\frac{15}{3} \text{ volts} \end{aligned}$$

$$\begin{aligned} \star) \text{ P.D. b/w points } A \text{ \& } C \text{ } (\Delta V_{AC}) &= (V_A - V_C) = (V_A - V_0) + (V_0 - V_C) \\ &= \left\{ -\frac{(q - q_1)}{C_1} \right\} + \left\{ \frac{q_1}{C_3} \right\} \\ &= -\frac{5}{3 \times 1} + \frac{5}{3} \\ \therefore \Delta V_{AC} &= 0 \text{ volt} \end{aligned}$$

$$\begin{aligned} \star) \text{ P.D. b/w points } B \text{ \& } C \text{ } (\Delta V_{BC}) &= (V_B - V_C) = (V_B - V_0) + (V_0 - V_C) \\ &= \left\{ \frac{q}{C_2} \right\} + \left\{ \frac{q_1}{C_3} \right\} \\ &= \frac{20}{3 \times 2} + \frac{5}{3} \\ \therefore \Delta V_{BC} &= 5 \text{ volt} \end{aligned}$$

$$\therefore \Delta V_{BC} = 5 \text{ volt}$$

$$\star) \text{ P.D. b/w points a \& o } (\Delta V_{DO}) = (V_D - V_O) = (V_D - V_B) + (V_B - V_O)$$

$$= -10 + \frac{q}{C_2}$$

$$= -10 + \frac{20}{3 \times 2}$$

$$= \frac{10}{3} - 10$$

$$\therefore \Delta V_{DO} = -20/3 \text{ volts}$$