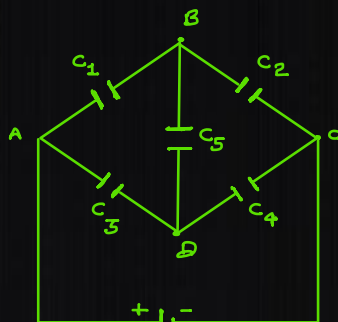


Wheat-Stone Bridge of Capacitors

24 July 2020 10:00

Wheat-stone Bridge is an apparatus to find the capacitance of any unknown capacitor.



A ; B ; C & D are junctions

(None of the 5 capacitors are in series or parallel)

case 1): Balanced Wheat-Stone Bridge: \rightarrow "In this case the potentials at the junctions which are not connected to the source are equal."

if ratio of the capacitance of the adjacent capacitors is found same


$$\text{i.e. } \frac{C_1}{C_2} = \frac{C_3}{C_4} \quad \text{or} \quad \frac{C_1}{C_3} = \frac{C_2}{C_4}$$

$$\text{Then ; } V_B = V_D$$

$$\text{i.e. } \Delta V_{BD} = 0$$

The capacitor C_5 becomes open circuit or no charge will be found on C_5 so we can remove it from the circuit

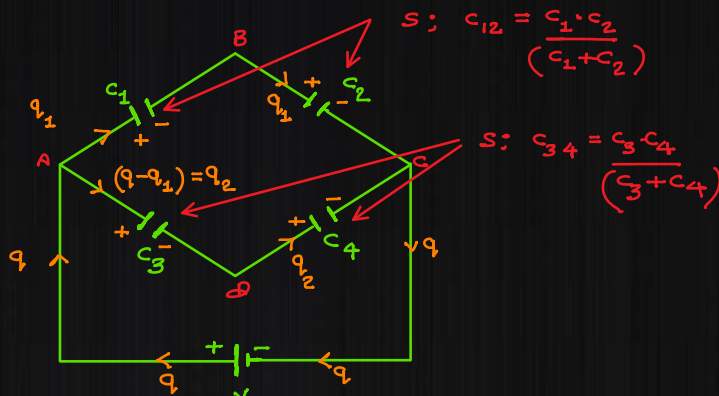\therefore The remaining circuit will look alike \rightarrow



$$S; C_{12} = \frac{C_1 \cdot C_2}{(C_1 + C_2)}$$

$$S; C_{34} = \frac{C_3 \cdot C_4}{(C_3 + C_4)}$$

\therefore equivalent capacitance b/w the points A & C (C_{eq}) = $C_{12} + C_{34}$

$$\Rightarrow C_{eq} = \frac{C_1 C_2}{(C_1 + C_2)} + \frac{C_3 C_4}{(C_3 + C_4)} \quad \text{--- ①}$$

charge flown through the battery (q) = $C_{eq} \cdot V$ --- ②

At junction A \rightarrow Distribution of charges takes place in the same ratio of the capacities

$$\therefore \frac{q_1}{q_2} = \frac{C_{12}}{C_{34}} \quad \text{also ; } q_1 + q_2 = q$$

$$\text{so charge in the capacitors } C_1 \text{ \& } C_2 (q_1) = \frac{C_{12} \cdot q}{(C_{12} + C_{34})} = \frac{C_{12} \cdot V}{(C_1 + C_2)} = \frac{C_1 \cdot C_2 \cdot V}{(C_1 + C_2)}$$


$$\text{f " " " " } C_3 \text{ \& } C_4 (q_2) = \frac{C_{34} \cdot q}{(C_{12} + C_{34})} = \frac{C_{34} \cdot V}{(C_3 + C_4)} = \frac{C_3 \cdot C_4 \cdot V}{(C_3 + C_4)}$$

this way we can find the energy stored in any capacitor as well as the p.d. across it.


eg: find the equivalent capacitance b/w points A & B.

P.D. across it.

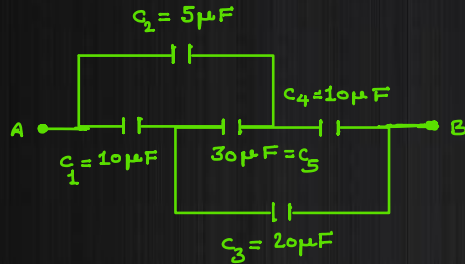eg: find the equivalent capacitance b/w points A & B.




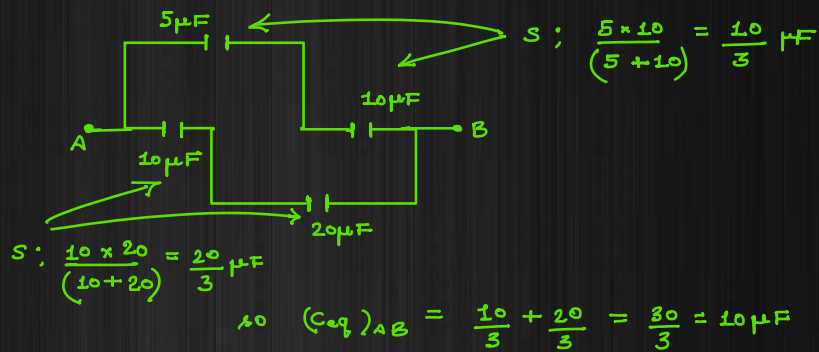
here; $\frac{C_1}{C_2} = \frac{C_3}{C_4}$ so the given wheatstone bridge is balanced
so we can remove C_5




eg:

Each capacitor is of $100 \mu F$ capacitance in the circuit shown below. If the ends A & B are connected across a 12 volt cell, find the

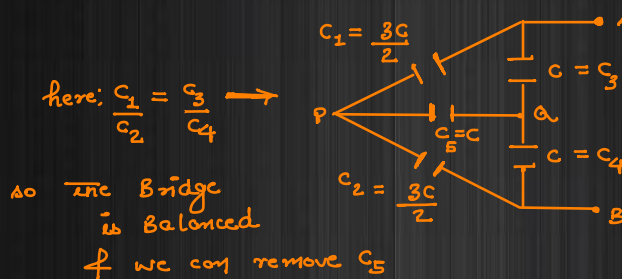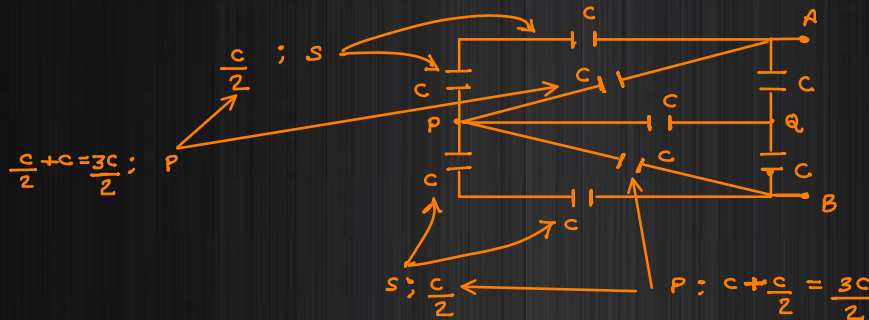- work done by the Battery
- energy stored in the capacitor system.
- equivalent capacitance b/w points A & B.



ie; $V_P = V_Q$

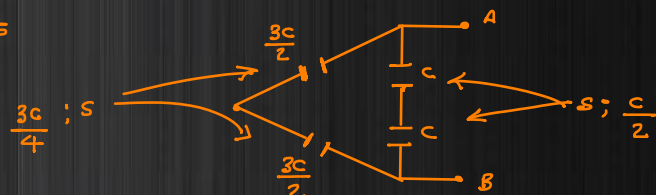

finally; $\frac{3C}{4}$ & $\frac{C}{2}$ are in parallel

$$\therefore (C_{eq})_{AB} = \frac{3C}{4} + \frac{C}{2} = \frac{5C}{4} = \frac{5}{4} \times 100 = 125 \mu F$$

\therefore charge flown through the Battery (q) = $C_{eq} \cdot V$

$$= 125 \times 12 = 1500 \mu C$$

so work done by the Battery (W_B) = $q \cdot V$

$$= 1500 \times 10^{-6} \times 12$$

$$= 18 \times 10^{-3} J = 18 mJ$$

\therefore Energy stored in the capacitor system (U_{sys}) = $\frac{1}{2} C_{eq} \cdot V^2$


$$= \frac{1}{2} \times 125 \times 10^{-6} \times (12)^2$$

$$= 9 \times 10^{-3} J$$

$$= 9 mJ = \frac{W_B}{2}$$

case 2: \rightarrow unbalanced wheatstone Bridge:

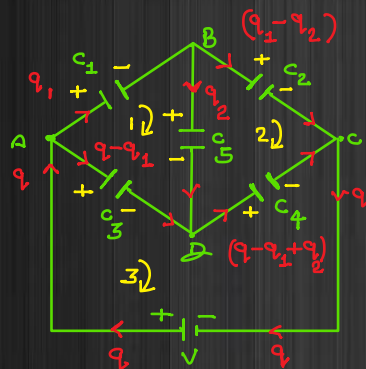in this case either the ratio of the capacities of the adjacent capacitors are not equal or P.D b/w the junctions not connected the Battery is found 0.



$$\text{if } \frac{C_1}{C_2} \neq \frac{C_3}{C_4}$$

then $V_B \neq V_D$ i.e. $\Delta V_{BD} \neq 0$

so C_5 cannot be open circuited.

The unbalanced wheat-stone bridge is analysed using Kirchhoff's laws.

Applying KVL in loop 1 A B D A

$$-\frac{q_1}{C_1} - \frac{q_2}{C_5} + \frac{(q_1 - q_2)}{C_3} = 0 \quad \text{--- (1)}$$

Applying KVL in loop 2 B C D B


$$-(\frac{q_1 - q_2}{C_2}) + (\frac{q_1 - q_2 + q_2}{C_4}) + \frac{q_2}{C_5} = 0 \quad \text{--- (2)}$$

Applying KVL in loop 3 A D C A

$$-(\frac{q - q_1}{C_3}) - (\frac{q - q_1 + q_2}{C_4}) + V = 0 \quad \text{--- (3)}$$

after solving eqn ①, ② & ③ we get the values of q , q_1 & q_2 which can be used to find the equivalent capacitance ($C_{eq} = \frac{q}{V}$), work done by the Battery ($W = q \cdot V$), charge & energy of any capacitor & the P.D. across any capacitor.

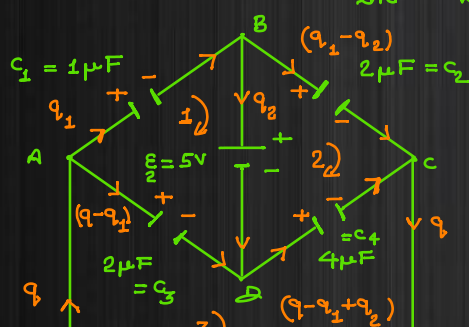eg: \rightarrow In the following circuit, find the following quantities after a long time the key shown has been closed.




i) Equivalent capacitance b/w A & C

ii) Work done by the Batteries 1 & 2

iii) P.D. b/w point D & C

iv) Energy stored in C_2 .

although $S_1 = S_2$ is applied but

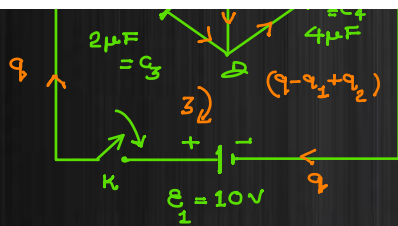

note: although $\frac{C_1}{C_2} = \frac{C_3}{C_4}$ is applied, but due to the 5V battery P.D. b/w B & D is not 0. so Bridge is not balanced.

Solⁿ:->

Applying KVL in loop 1 A B D A

$$\begin{aligned} -\frac{q_1}{1} - 5 + \frac{(q - q_1 + q_2)}{2} &= 0 \\ \Rightarrow -2q_1 - 10 + q - q_1 &= 0 \\ \Rightarrow q - 3q_1 &= 10 \quad \text{--- (1)} \end{aligned}$$

Applying KVL in loop 2, B C D B

$$\begin{aligned} -\left(\frac{q_1 - q_2}{2}\right) + \frac{(q - q_1 + q_2)}{4} + 5 &= 0 \\ \Rightarrow -2q_1 + 2q_2 + q - q_1 + q_2 + 20 &= 0 \\ \Rightarrow 3q_2 - 3q_1 - q &= 20 \quad \text{--- (2)} \end{aligned}$$

Applying KVL in loop 3, A D C A

$$\begin{aligned} -\left(\frac{q - q_1}{2}\right) - \frac{(q - q_1 + q_2)}{4} + 10 &= 0 \\ \Rightarrow -2q + 2q_1 - q + q_1 - q_2 + 40 &= 0 \\ \Rightarrow 3q + q_2 - 3q_1 &= 40 \quad \text{--- (3)} \end{aligned}$$

$$\begin{aligned} \text{eqn (1) + (2)} \\ -3q_2 &= 30 \end{aligned}$$

charge flown through C_2 $\Rightarrow q_2 = -10 \mu\text{C}$ (4) $\left(\because \text{the charge in the branch is found -ve, so we can say in fact } +10 \mu\text{C charge is flowing from D to C.} \right)$

from (3) & (4)

$$\begin{aligned} 3q - 10 - 3q_1 &= 40 \\ \Rightarrow 3q - 3q_1 &= 50 \quad \text{--- (5)} \end{aligned}$$

$$\text{eqn (5) - (1)}$$

$$3q - 3q_1 = 50$$

$$\begin{aligned} \frac{q - 3q_1}{+} &= \frac{10}{-} \\ 2q &= 40 \end{aligned}$$

charge flown through Battery 1 $\Rightarrow q = 20 \mu\text{C}$ (6) so from (1) again:

$$20 - 3q_1 = 10$$

$$q_1 = \frac{10}{3} \mu\text{F} \quad \text{--- (7)}$$

so; equivalent capacity b/w A & C: $(C_{eq}) = \frac{q}{E_1} = \frac{20 \times 10^{-6}}{10} = 2 \mu\text{F}$

$$\text{work done by Battery 1 } (W_{B1}) = q \cdot E_1 = 20 \times 10^{-6} \times 10 = 2 \times 10^{-4} \text{ J} = 0.2 \text{ mJ}$$

$$,, ,, ,, ,, 2 (W_{B2}) = q_2 \cdot E_2 = 10 \times 10^{-6} \times 5 = 5 \times 10^{-5} \text{ J} = 0.05 \text{ mJ}$$

$$\text{P.D. b/w point D & C } (\Delta V_{DC}) = \frac{(q - q_1 + q_2)}{C_4}$$

$$= \frac{20 - \frac{10}{3} + (-10)}{4} = \frac{20}{12} = \frac{5}{3} = 1.67 \text{ volt}$$

Energy stored in $C_2 : \rightarrow$

$$U_{C_2} = \frac{1}{2} \times \frac{(q_1 - q_2)^2}{C_2}$$

$$= \frac{1}{2} \times \left[\frac{10}{3} - (-10) \right]^2 \times 10^{-12}$$

$$= \frac{1}{2} \times \left(\frac{40}{3} \right)^2 \times 10^{-12}$$

$$= \frac{400}{9} \times 10^{-12} \text{ J}$$

$$\Rightarrow U_{C_2} = \frac{400}{9} \mu\text{J}$$