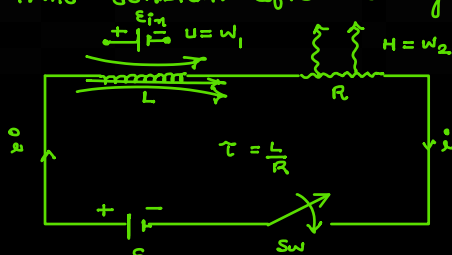


Self & Mutual Induction

22 September 2020

17:00

Q:→ In the following circuit find the work done by the battery in one time constant after closing the switch.



Sol:→

instantaneous charging current in the circuit:

$$i = \frac{\varepsilon}{R} \cdot \left\{ 1 - e^{-\frac{Rt}{L}} \right\} \quad \text{--- (1)}$$

∴ conservative part of work done by the battery get stored in form of P.E. on the axis of the inductor coil.

$$W_1 = U = \frac{1}{2} Li^2$$

$$= \frac{1}{2} \cdot L \cdot \frac{\varepsilon^2}{R^2} \cdot \left(1 - e^{-\frac{Rt}{L}} \right)^2$$

$$\text{at } t = \frac{L}{R} \text{ or } \tau$$

$$= \frac{1}{2} \cdot L \cdot \frac{\varepsilon^2}{R^2} \cdot \left\{ 1 - e^{-\frac{R}{L} \cdot \frac{L}{R}} \right\}^2$$

$$= \frac{\varepsilon^2 L}{2R^2} \cdot \left\{ 1 - e^{-1} \right\}^2$$

$$\therefore W_1 = \frac{\varepsilon^2 L}{2R^2} \cdot \left\{ 1 + e^{-2} - 2e^{-1} \right\} \quad \text{--- (1)}$$

non-conservative part of work get lost in form of heat across the resistor

$$\therefore W_2 = H = \int_0^{\tau} i^2 \cdot R \cdot dt$$

$$= \int_0^{\tau} \frac{\varepsilon^2}{R^2} \cdot \left(1 - e^{-\frac{Rt}{L}} \right)^2 \cdot R \cdot dt$$

$$= \frac{\varepsilon^2}{R} \cdot \int_0^{\tau} \left\{ 1 + e^{-\frac{2t}{\tau}} - 2 \cdot e^{-\frac{t}{\tau}} \right\} \cdot dt$$

$$= \frac{\varepsilon^2}{R} \cdot \left[t + \frac{e^{-\frac{2t}{\tau}}}{\left(-\frac{2}{\tau}\right)} - 2 \cdot \frac{e^{-\frac{t}{\tau}}}{\left(-\frac{1}{\tau}\right)} \right]_0^{\tau}$$

$$= \frac{\varepsilon^2}{R} \cdot \left[\left\{ \tau - \frac{\tau}{2} \cdot e^{-2} + 2\tau \cdot e^{-1} \right\} - \left\{ 0 - \frac{\tau}{2} \cdot e^0 + 2\tau \cdot e^0 \right\} \right]$$

$$= \frac{\varepsilon^2}{R} \cdot \left[\tau - \frac{\tau}{2} \cdot e^{-2} + 2\tau \cdot e^{-1} + \frac{\tau}{2} - 2\tau \right]$$

$$= \frac{\varepsilon^2}{R} \cdot \left[-\frac{\tau}{2} - \frac{\tau}{2} \cdot e^{-2} + 2\tau \cdot e^{-1} \right]$$

$$= \frac{\varepsilon^2}{R} \cdot \frac{L}{2R} \cdot \left\{ -1 - e^{-2} + 4e^{-1} \right\}$$

$$\Rightarrow W_2 = \frac{\varepsilon^2 L}{2R^2} \cdot \left\{ -1 - e^{-2} + 4e^{-1} \right\} \quad \text{--- (2)}$$

$$\text{eqn (1) + (2)}$$

$$\therefore W = W_1 + W_2$$

$$= \frac{\varepsilon^2 L}{2R^2} \cdot \left\{ 1 + e^{-2} - 2e^{-1} - 1 - e^{-2} + 4e^{-1} \right\}$$


$$= \frac{\varepsilon^2 L}{2R^2} \cdot 2 \cdot e^{-1}$$

$$\therefore W = \frac{\varepsilon^2 L}{eR^2} \text{ Joules}$$

Q:→ find the time constant & steady-state current in the following circuit

$$\therefore W = \frac{\varepsilon \cdot L}{e R^2} \text{ Joules}$$

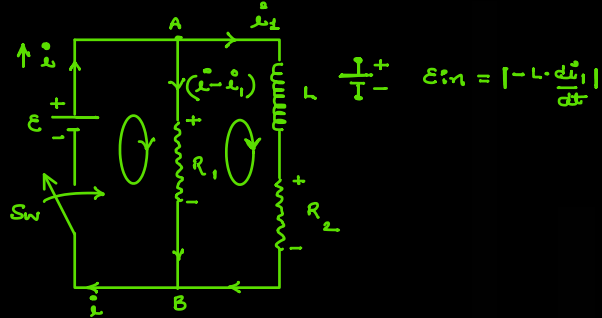Q: → find the time constant & steady-state current in the following circuit.



Solⁿ: →

KVL in loop 1: →

$$-(i - i_1) \cdot R_1 + \varepsilon = 0$$

$$\Rightarrow (i - i_1) \cdot R_1 = \varepsilon \quad \text{--- (1)}$$

KVL in loop 2: →

$$\Rightarrow -L \cdot \frac{di_2}{dt} - i_1 \cdot R_2 + (i - i_1) \cdot R_1 = 0$$

from eqn (1):

$$-L \cdot \frac{di_2}{dt} - i_1 \cdot R_2 + \varepsilon = 0$$

$$\Rightarrow L \cdot \frac{di_2}{dt} = \varepsilon - i_1 \cdot R_2$$

$$\Rightarrow \int_0^t \left(\frac{di_2}{\varepsilon - i_1 \cdot R_2} \right) = \int_0^t \frac{dt}{L}$$

$$\Rightarrow \left\{ -\frac{1}{R_2} \cdot \log_e (\varepsilon - i_1 \cdot R_2) \right\}_0^t = \left(\frac{t}{L} \right)_0^t$$

$$\Rightarrow \log_e (\varepsilon - i_1 \cdot R_2) - \log_e \varepsilon = -\frac{R_2}{L} \cdot (t - 0)$$

$$\Rightarrow \log_e \left\{ \frac{\varepsilon - i_1 \cdot R_2}{\varepsilon} \right\} = -\frac{R_2}{L} \cdot t$$

$$\Rightarrow \left(\frac{\varepsilon - i_1 \cdot R_2}{\varepsilon} \right) = e^{-\frac{R_2}{L} \cdot t}$$

$$\Rightarrow \varepsilon - i_1 \cdot R_2 = \varepsilon \cdot e^{-\frac{R_2}{L} \cdot t}$$

$$\Rightarrow i_1 = \frac{\varepsilon}{R_2} \cdot \left\{ 1 - e^{-\frac{R_2}{L} \cdot t} \right\}$$

$$\text{here } \tau = \frac{L}{R_2}$$

from eqn (1)


$$i \cdot R_1 = \varepsilon + i_1 \cdot R_1$$

$$\therefore i = \frac{\varepsilon}{R_1} + \frac{\varepsilon}{R_2} \cdot \left(1 - e^{-\frac{R_2}{L} \cdot t} \right)$$

inst. current from the battery

Method 2: →

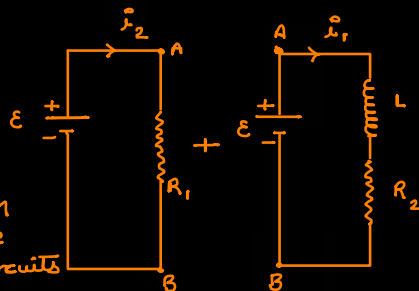
Given circuit can be written as superposition of these 2 circuits




$$i_2 = \frac{\varepsilon}{R_1} ; i_1 = \frac{\varepsilon}{R_2} \cdot \left(1 - e^{-\frac{R_2}{L} \cdot t} \right)$$


$$\therefore i = i_1 + i_2 = \frac{\varepsilon}{R_1} + \frac{\varepsilon}{R_2} \cdot \left(1 - e^{-\frac{R_2}{L} \cdot t} \right)$$

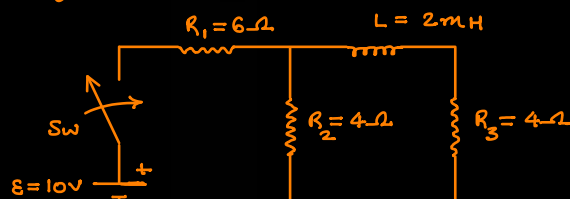Q: find the ratio of the initial to the steady state currents



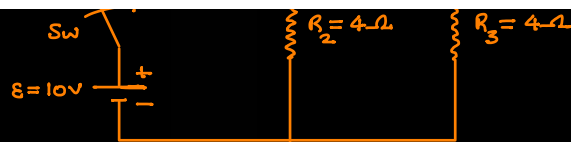

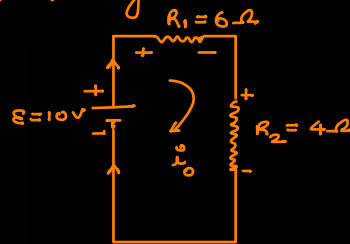
Solⁿ: at $t=0$; initially inductor is open circuit



$$i_0 = \frac{\mathcal{E}}{R_{eq}} = \frac{\mathcal{E}}{R_1 + R_2} = \frac{10}{10}$$

$$i_0 = 1 \text{ Amp} \quad \text{--- (1)}$$

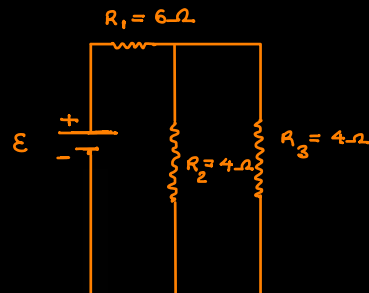at $t \rightarrow \infty$; inductor coil becomes short circuit




$$i_{\infty} = \frac{\mathcal{E}}{R_{eq}} = \frac{\mathcal{E}}{R_1 + R_{23}} = \frac{10}{6+2}$$


$$i_{\infty} = \frac{5}{4} \text{ A}$$

$$\therefore \frac{i_0}{i_{\infty}} = \frac{4}{5} \quad \text{--- (2)}$$

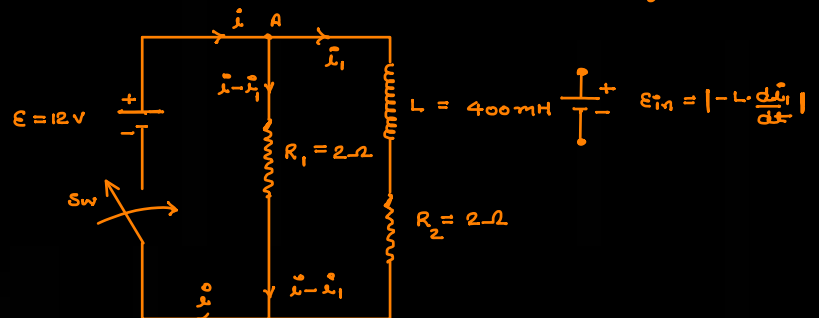Q:→ find the p.d. across the inductor coil as a fn. of time t .



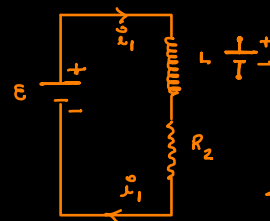Solⁿ: as p.d. across A & B is \mathcal{E} ; we can consider the circuit as:



here: $i_1 = \frac{\mathcal{E}}{R_2} \cdot (1 - e^{-R_2 \cdot t / L})$

$$\mathcal{E}_{in} = \left| -L \cdot \frac{di_1}{dt} \right|$$


$$= \left| -L \cdot \frac{\mathcal{E}}{R_2} \cdot (0 - e^{-R_2 \cdot t / L} \cdot -\frac{R_2}{L}) \right|$$

$$\Rightarrow \mathcal{E}_{in} = \mathcal{E} \cdot e^{-\frac{R_2 \cdot t}{L}}$$

$$= 12 \cdot e^{-\frac{2 \times t}{0.4}}$$

$$\mathcal{E}_{in} = 12 \cdot e^{-5t}$$

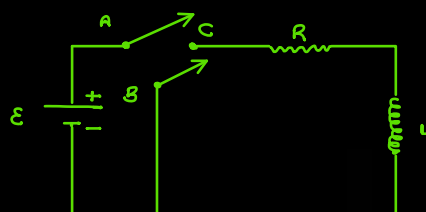Q:→ initially point A & C were connected for a long time, then it is disconnected & B & C are connected at $t=0$. Find the ratio of the voltages about the resistor & the inductor at $t = \frac{L}{R}$.



Solⁿ: when A & C were connected for a long time (charging

Solⁿ: \rightarrow when a & c were connected for a long time (charging state)

$$i = \frac{\varepsilon}{R} \cdot (1 - e^{-\frac{Rt}{L}})$$

at $t \rightarrow \infty$ (steady state)

$$i = \frac{\varepsilon}{R} = i_0 \quad \text{--- (1)}$$

when b & c are connected (Discharging state)

$$\text{Discharging current } (i) = i_0 \cdot e^{-\frac{Rt}{L}}$$

$$\therefore \text{P.D. across the resistor } (\Delta V_R) = i \cdot R$$

$$= i_0 \cdot R \cdot e^{-\frac{Rt}{L}}$$

$$\Delta V_R = \varepsilon \cdot e^{-\frac{Rt}{L}} \quad \text{--- (2)}$$

inst. P.D. across the inductor

$$\Delta V_L = \left| -L \cdot \frac{di}{dt} \right|$$

$$= \left| -L \cdot \frac{\varepsilon}{R} \cdot e^{-\frac{Rt}{L}} \times -\frac{R}{L} \right|$$

$$\Delta V_L = \varepsilon \cdot e^{-\frac{Rt}{L}} \quad \text{--- (3)}$$

$$\therefore \frac{\Delta V_R}{\Delta V_L} = 1$$

Q: \rightarrow A smooth conducting frame ABCD is kept in the vertical plane. A conducting rod of mass m can slide over it remaining always horizontal. There is no resistance in the loop & its inductance is L . Initially, no current was there in the circuit. The rod is allowed to fall under gravity & a uniform magnetic field exists perpendicular to the plane. find: i) maximum velocity of the rod.

ii) Maximum current in the circuit

Solⁿ: \rightarrow

as the rod & inductor are in parallel

$$\therefore (\varepsilon_{in}) = (\varepsilon_{in})$$

S.I. Mot


$$\Rightarrow L \cdot \frac{di}{dt} = B \cdot v \cdot l \sin 90^\circ$$

$$\Rightarrow L \cdot \frac{di}{dt} = B \cdot v \cdot l$$

$$\Rightarrow L \cdot \frac{di}{dt} = B \cdot \frac{dx}{dt} \cdot l$$

$$\Rightarrow L \cdot \int_0^i di = B \cdot l \cdot \int_0^x dx$$
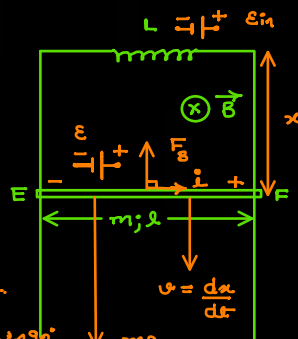
$$\Rightarrow L \cdot i = B \cdot l \cdot x \quad \text{--- (1)}$$



$$\therefore mg - F_B = m \cdot a$$

$$mg - i \cdot B \cdot l \sin 90^\circ = m \cdot a \quad \text{--- (2)}$$

as v becomes maximum

$$a = 0$$

$$mg - i B l = 0$$

$$\text{current } \Rightarrow i = \frac{mg}{B \cdot l} \quad \text{--- (3)}$$

where velocity becomes max.

from (1)

$$x_M = \frac{L \cdot mg}{B \cdot l^2}$$

$$\text{position } x_M = \frac{mgL}{B^2 \cdot l^2} \quad \text{--- (4)}$$

where velocity becomes max.

from (1) & (2)

$$mg - \frac{B^2 \cdot l^2}{L} \cdot x = m \cdot v \cdot \frac{dv}{dx}$$

$$mg \int_0^{x_M} dx - \frac{B^2 \cdot l^2}{L} \int_0^{x_M} x \cdot dx = m \int_0^{v_M} v \cdot dv$$

$$\Rightarrow mg \cdot x_M - \frac{B^2 \cdot l^2}{L} \cdot \frac{x_M^2}{2} = m \cdot \frac{v_M^2}{2}$$

$$\Rightarrow mg \cdot x_M - \frac{B^2 \cdot l^2}{L} \cdot \frac{x_M^2}{2} = m \cdot \frac{v_M^2}{2}$$

from ④

$$mg \cdot \frac{mg \cdot L}{B^2 \cdot l^2} - \frac{B^2 \cdot l^2}{L} \cdot \frac{m^2 \cdot g^2 \cdot L^2}{2 \cdot B^4 \cdot l^4} = \frac{m v_M^2}{2}$$

$$\Rightarrow \frac{m^2 \cdot g^2 \cdot L}{B^2 \cdot l^2} - \frac{m^2 \cdot g^2 \cdot L}{2 \cdot B^2 \cdot l^2} = \frac{m v_M^2}{2}$$

$$\Rightarrow \frac{m^2 \cdot g^2 \cdot L}{2 \cdot B^2 \cdot l^2} = \frac{m v_M^2}{2}$$

$$\therefore v_M^2 = \frac{m \cdot g^2 \cdot L}{B^2 \cdot l^2}$$

$$\therefore v_M = \frac{g \cdot \sqrt{mL}}{Bl} \text{ m/s}$$

Max.
velocity

from ① & ④


$$e_M = \frac{B \cdot l \cdot x_M}{L}$$

$$= \frac{Bl}{L} \cdot \frac{mg \cdot L}{B^2 l^2}$$

Max. current $i_M = \frac{mg}{Bl}$


Q:→ A coil of inductance $L = 2\mu\text{H}$ & resistance $R = 1\Omega$ is connected as shown in the fig. EMF of the battery is $\mathcal{E} = 3\text{V}$ & the resistance R_0 is of 2Ω . Find the heat generated in resistor R_0 after the switch is disconnected.

Soln:→

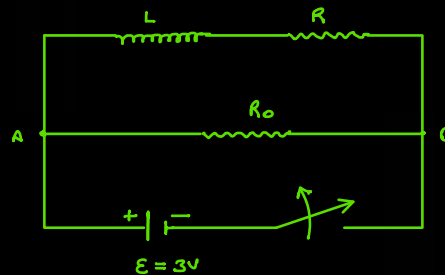

during the charging state:

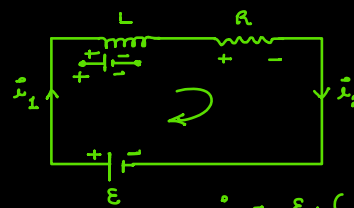as the L - R & \mathcal{E} are directly in parallel




$$i_1 = \frac{\mathcal{E}}{R} \cdot (1 - e^{-\frac{R \cdot t}{L}}) \quad \text{instantaneous charging current}$$


at steady state;

$$i_1 = \frac{\mathcal{E}}{R} \cdot (1 - e^{-\infty})$$

$$(i_1)_{\text{Max}} = \frac{\mathcal{E}}{R} \quad ; \quad \text{Max. current through the inductor}$$

during the discharging state;

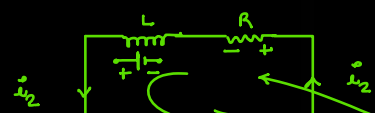

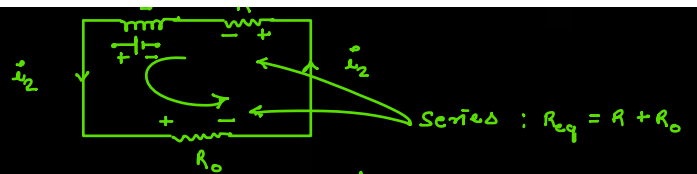

instantaneous discharging current:

$$i_2 = (i_1)_{\text{max}} \cdot e^{-R_{\text{eq}} \cdot \frac{t}{L}}$$

$$i_2 = \frac{\varepsilon}{R} \cdot e^{-\frac{(R_0 + R) \cdot t}{L}} \quad \text{--- (2)}$$

∴ heat generated across R_0 during the discharge

$$H = \int_0^{\infty} i_2^2 \cdot R_0 \cdot dt$$

$$= \frac{\varepsilon^2}{R^2} \cdot R_0 \cdot \int_0^{\infty} e^{-2(R_0 + R) \cdot \frac{t}{L}} \cdot dt$$

$$= \frac{\varepsilon^2 \cdot R_0}{R^2} \cdot \left\{ e^{-2(R_0 + R) \cdot \frac{t}{L}} \cdot \frac{-L}{2(R_0 + R)} \right\}_0^{\infty}$$


$$= \frac{\varepsilon^2 \cdot R_0}{2R^2 (R_0 + R)} \cdot \{ e^0 - e^{-\infty} \}$$

$$= \frac{\varepsilon^2 \cdot R_0 \cdot L}{2R^2 (R_0 + R)}$$

$$= \frac{9 \times 2 \times 2 \times 10^{-6}}{2 \times 1^2 \times 3}$$

$$\therefore H = 6 \mu\text{J}$$

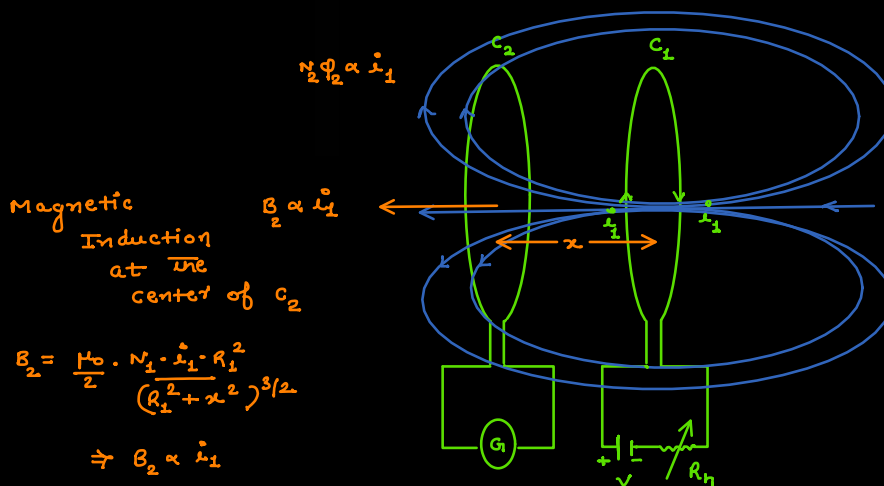Mutual Inductance → In this type of EMI, EMF & current are induced in any coil by changing the current in any nearby coil.



flux linked to the 2nd coil \propto current in the 1st coil

$$N_2 \Phi_2 \propto i_1$$

$$N_2 \cdot \Phi_2 = M_{21} \cdot i_1 \quad \text{--- (1)}$$

coefficient of mutual induction of C_2 w.r.t C_1

$$M_{21} = \frac{N_2 \cdot \Phi_2}{i_1} \quad \text{Henry ; } [ML^2T^{-2}A^{-2}]$$

it depends upon the shape, size, material & the surrounding medium.

from Faraday's Law:

$$\varepsilon_2 = -N_2 \cdot \frac{d\Phi_2}{dt} \quad \text{--- (2)}$$

Differentiating eqn (1):

Differentiating eqn ①;

$$N_2 \cdot \frac{d\phi_2}{dt} = M_{21} \cdot \frac{di_1}{dt} \quad \text{--- ③}$$

from ② & ③

Mutually induced EMF in C_2 $\boxed{\varepsilon_2 = -M_{21} \cdot \frac{di_1}{dt}}$ volt --- ④

current induced in C_2 due to mutual induction

$$i_2 = \frac{\varepsilon_2}{R_2} = -\frac{M_{21}}{R_2} \cdot \frac{di_1}{dt} \quad \text{--- ⑤}$$

note: 1) due to change in current in C_1 , self induction takes place in C_1 itself.

self induced EMF in C_2 ; $\varepsilon_1 = -L_1 \cdot \frac{di_1}{dt}$

2) if currents in both the nearby coils are changing.


total induced EMFs in the coils

$\varepsilon_1 = (\varepsilon_1)_{\text{self}} + (\varepsilon_1)_{\text{mutual}}$

$\therefore \varepsilon_1 = \left(-L_1 \cdot \frac{di_1}{dt}\right) + \left(-M_{12} \cdot \frac{di_2}{dt}\right)$

$\varepsilon_2 = (\varepsilon_2)_{\text{self}} + (\varepsilon_2)_{\text{mutual}}$

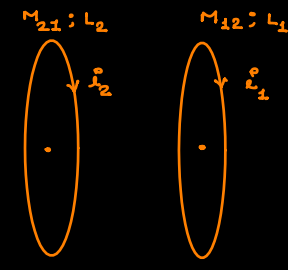$= \left(-L_2 \cdot \frac{di_2}{dt}\right) + \left(-M_{21} \cdot \frac{di_1}{dt}\right)$




Q: find the coefficient of mutual induction of the following two concentric coplanar coils. Here $r_1 \ll r_2$

Solⁿ:→

flux linked to each turn of C_1
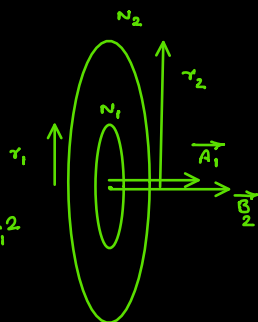
$$\begin{aligned} \phi_1 &= \vec{B}_2 \cdot \vec{A}_1 \\ &= B_2 \cdot A_1 \cdot \cos 0^\circ \\ &= \frac{\mu_0}{2} \cdot N_2 \cdot \frac{i_2}{r_2} \cdot \pi r_1^2 \end{aligned}$$



so coeff. of mutual induction of C_1 w.r.t. C_2 (M_{12}) = $\frac{N_1 \cdot \phi_1}{i_2}$

$$M_{12} = \frac{\mu_0 \cdot \pi \cdot N_1 \cdot N_2 \cdot r_1^2}{2 r_2} \quad \text{H} \quad \text{--- ①}$$

flux linked to each turn of C_2 (ϕ_2) = $\vec{B}_1 \cdot \vec{A}_2$

} area of the smaller coil will be again taken into account

$$\phi_2 = \frac{\mu_0}{2} \cdot \frac{N_1 \cdot i_1}{r_1} \cdot \pi r_1^2$$

\therefore coeff. of mutual induction of C_2 w.r.t. C_1

$$M_{21} = \frac{N_2 \cdot \phi_2}{i_1} = \frac{\mu_0 \cdot N_1 \cdot N_2 \cdot \pi r_1^2}{2 r_1} \quad \text{H} \quad \text{--- ②}$$

eqn ① & ②

$$M_{12} = M_{21} = \mu_0 \cdot \pi \cdot N_1 \cdot N_2 \cdot r_1$$

$$\frac{e_{\gamma_1} \textcircled{1}}{p} \textcircled{2}$$

$$\frac{m_1}{m_2} = \frac{a_1}{a_2}$$