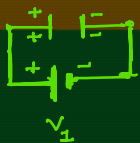


Charge distribution between capacitors

15 July 2020 11:30


Step 1: \Rightarrow initially we charged both the capacitors with the help of Batteries.

$$C_1 \quad 0 \rightarrow q_1$$



$$q_1 = C_1 \cdot V_1 \quad \text{--- (1)}$$

$$C_2 \quad 0 \rightarrow q_2$$

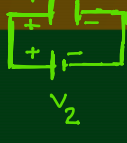

$$q_2 = C_2 \cdot V_2 \quad \text{--- (2)}$$

initial charges on both the capacitors

note: if the 2nd capacitor is uncharged take $V_2 = 0$

Let after some time the common potential of both the capacitor becomes 'V'.

$$\therefore \text{final charge on } C_1 (q'_1) = C_1 \cdot V \quad \text{--- (3)}$$

$$\text{f " " " } C_2 (q'_2) = C_2 \cdot V \quad \text{--- (4)}$$

from conservation of charge:

$$(q_{\text{sys}})_i = (q_{\text{sys}})_f$$

$$q_1 + q_2 = q'_1 + q'_2$$

$$\Rightarrow C_1 \cdot V_1 + C_2 \cdot V_2 = C_1 \cdot V + C_2 \cdot V$$

$$\text{final P.D. } \Rightarrow V = \frac{(C_1 V_1 + C_2 V_2)}{(C_1 + C_2)} \text{ volt --- (*)}$$

b/w the plates of each capacitor

from eqn (3) f (4)

$$\text{final charge on } C_1 = C_1 \cdot \frac{(C_1 V_1 + C_2 V_2)}{(C_1 + C_2)}$$

$$\text{" " " } C_2 = C_2 \cdot \frac{(C_1 V_1 + C_2 V_2)}{C_1 + C_2}$$


very imp. concept: During redistribution of charges b/w only two or more capacitors, the final charges are found in the same ratio of their capacities.

$$\text{ie: } \frac{q'_1}{q'_2} = \frac{C_1 \cdot V}{C_2 \cdot V} = \frac{C_1}{C_2} \quad \text{--- (*)}$$

Most imp concept: \Rightarrow change in energy of the system during redistribution.

Step 2: \Rightarrow The we disconnect them from sources f connect them together.

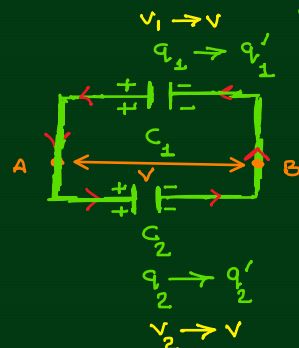
case (1): \Rightarrow plates having same polarities are connected together.



charge will start from the capacitor at higher potential to the capacitor at lower potential.

This charge flow takes place until both the capacitors comes at a common potential ie the P.D. b/w them becomes zero.

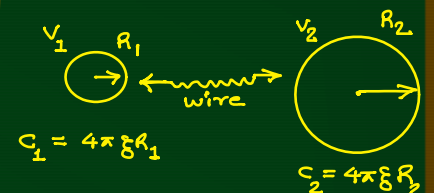for isolated pair of spherical capacitors



$$C_1 = 4\pi\epsilon_0 R_1$$

$$C_2 = 4\pi\epsilon_0 R_2$$

$$\therefore V = \frac{C_1 \cdot V_1 + C_2 \cdot V_2}{C_1 + C_2}$$

$$\Rightarrow V = \frac{(R_1 \cdot V_1 + R_2 \cdot V_2)}{R_1 + R_2}$$

final potential on both the spheres

$$\text{also: } \frac{q'_1}{q'_2} = \frac{C_1}{C_2} = \frac{R_1}{R_2}$$

Most imp concept : \rightarrow change in energy of the system during redistribution.

$$\begin{aligned}\Delta U &= (U_f)_{sys} - (U_i)_{sys} \\ &= \left[\frac{1}{2} C_1 V^2 + \frac{1}{2} C_2 V^2 \right] - \left[\frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 \right] \\ &= \frac{1}{2} \left[(C_1 + C_2) \cdot \left\{ \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} \right\}^2 - (C_1 V_1^2 + C_2 V_2^2) \right] \\ &= \frac{1}{2} \left[\frac{(C_1 V_1 + C_2 V_2)^2}{(C_1 + C_2)} - C_1 V_1^2 - C_2 V_2^2 \right] \\ &= \frac{1}{2} \cdot \left[\frac{C_1^2 V_1^2 + C_2^2 V_2^2 + 2 C_1 C_2 V_1 V_2 - C_1^2 V_1^2 - C_1 C_2 V_2^2 - C_1 C_2 V_1^2 - C_2^2 V_2^2}{C_1 + C_2} \right] \\ &= \frac{-C_1 C_2}{2(C_1 + C_2)} \cdot \{ V_1^2 + V_2^2 - 2 V_1 V_2 \}\end{aligned}$$

$$\Rightarrow \boxed{\Delta U_{sys} = \frac{-C_1 C_2}{2(C_1 + C_2)} \cdot (V_1 - V_2)^2} = \text{always } -ve$$


\therefore There is always a loss in energy during the redistribution of charges b/w capacitors in form of heat

Loss of Energy or Heat liberated

$$H = \frac{C_1 \cdot C_2 \cdot (V_1 - V_2)^2}{2(C_1 + C_2)} \text{ Joules} \quad \text{---} \star$$

Case ② : \rightarrow if the plates of opposite polarity are connected together.

$$\begin{aligned}q_1 &= C_1 \cdot V_1 \quad \rightarrow \quad \begin{array}{|c|} \hline + \\ \hline \end{array} \quad \begin{array}{|c|} \hline - \\ \hline \end{array} \\ q_2 &= -C_2 \cdot V_2 \quad \rightarrow \quad \begin{array}{|c|} \hline - \\ \hline \end{array} \quad \begin{array}{|c|} \hline + \\ \hline \end{array} \\ &\quad \quad \quad -V_2\end{aligned}$$

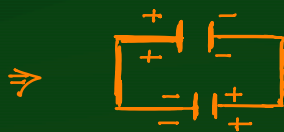

$$C_1 : q_1 \rightarrow q'_1 ; V_1 \rightarrow V$$

$$C_2 : q_2 \rightarrow q'_2 ; V_2 \rightarrow V$$

$$q_1 + q_2 = q'_1 + q'_2$$

$$C_1 V_1 - C_2 V_2 = C_1 V + C_2 V$$

common potential finally on each capacitor

$$\rightarrow V = \frac{(C_1 V_1 - C_2 V_2)}{(C_1 + C_2)} \quad \text{---} \textcircled{1}$$

$$\begin{aligned}\therefore \text{ final charge on } C_1 &= q'_1 \text{ or } C_1 \cdot V = C_1 \cdot \frac{(C_1 V_1 - C_2 V_2)}{(C_1 + C_2)} \\ \text{" " " } C_2 &= q'_2 \text{ or } C_2 \cdot V = C_2 \cdot \frac{(C_1 V_1 - C_2 V_2)}{(C_1 + C_2)}\end{aligned}$$

$$\Rightarrow \boxed{\frac{q'_1}{q'_2} = \frac{C_1}{C_2}} \quad \text{---} \star$$

in this case change in P.E. of the system.

$$\Delta U = \frac{-C_1 C_2}{2(C_1 + C_2)} \cdot (V_1 + V_2)^2 \text{ J}$$

$$\text{heat appeared } H = \frac{C_1 C_2}{2(C_1 + C_2)} \cdot (V_1 + V_2)^2 \text{ Joules.}$$

$$U = \frac{1}{2} C V^2 = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} Q \cdot V$$

$$U = \frac{1}{2} C V^2 = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} Q \cdot V$$

$$\downarrow C = \frac{\epsilon A}{d} \uparrow$$

More heat loss will take place in this case


$$\text{heat appeared } H = \frac{C_1 C_2}{2(C_1 + C_2)} \cdot (V_1 + V_2)^2 \text{ Joules.}$$

Q: \rightarrow Each plate of a parallel plate air capacitor is of area 'S'. What amount of work done has to be performed to slowly increase the distance b/w the plates from x_1 to x_2 if \rightarrow

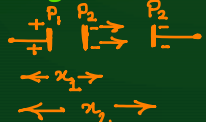i) The charge on the plates is 'Q' is kept const. ii) P.D. b/w the plates 'V' is kept const.

$$\Rightarrow W_{\text{ext}} = -W_{\text{elec}} = -(C \Delta U)$$

$$\Rightarrow W_{\text{ext}} = \Delta U \quad \text{or} \quad (U_f - U_i)$$



$$\text{i) } W_{\text{ext}} = U_f - U_i = \frac{1}{2} \frac{Q^2}{C_2} - \frac{1}{2} \frac{Q^2}{C_1}$$

$$\therefore C = \frac{\epsilon \cdot S}{x}$$

$$W_{\text{ext}} = \frac{Q^2}{2\epsilon S} \cdot \left\{ \frac{x_2}{2} - \frac{x_1}{2} \right\} \text{ J}$$

$$\text{ii) } W_{\text{ext}} = U_f - U_i = \frac{1}{2} C_2 V^2 - \frac{1}{2} C_1 V^2$$

$$W_{\text{ext}} = \frac{V^2}{2} \left(\frac{\epsilon S}{x_2} - \frac{\epsilon S}{x_1} \right) = \frac{\epsilon \cdot S \cdot V^2}{2x_1 x_2} (x_1 - x_2)$$


Q: A parallel plate capacitor having capacity C & dielectric const. K is charged upto a potential difference V. The Dielectric slab is then removed slowly then the battery is disconnected & again the slab is re-inserted b/w the plates. Find the Total work done in this process.

Solⁿ: \rightarrow

$$\text{if } C_{\text{air}} = C$$

$$\text{Then } C_d = K \cdot C$$
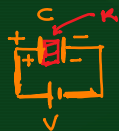
$$\begin{aligned} & +\sigma \quad -\sigma \\ & \downarrow \quad \downarrow \\ & +\sigma \quad -\sigma \\ & \sigma_p = \sigma \left(1 - \frac{1}{K}\right) \end{aligned}$$



i) work done during removal of Dielectric in presence of Batt.

$$(W_1)_{\text{ext}} = \Delta U = U_f - U_i = \frac{1}{2} C_{\text{air}} \cdot V^2 - \frac{1}{2} C_d \cdot V^2 = \frac{C}{2} (1-K) \cdot V^2 = -ve$$

ii) Now the battery is disconnected \rightarrow

as the charge remaining after the Dielectric comes out

$$Q = C_{\text{air}} \cdot V = C \cdot V = \text{const}$$

$$(W_2)_{\text{ext}} = \Delta U = U_f - U_i$$

$$= \frac{1}{2} \frac{Q^2}{C} - \frac{1}{2} \frac{Q^2}{C_d} = \frac{C^2 V^2}{2} \left\{ \frac{1}{K} - \frac{1}{C} \right\} = \frac{C V^2}{2K} (1-K) = \frac{C V^2}{2K} (1-K) \left(1 + \frac{1}{K}\right) = -ve$$

Q: \rightarrow A parallel plate capacitor have plate area 100cm^2 & gap 2cm b/w the plates. It is charged upto 300volts . if the plates are moved apart to a distance 5cm without disconnecting the power source. find

i) Electric charge flown from the source

ii) work done required

iii) find the work required to increase the gap after removing the battery.

Solⁿ: \rightarrow keeping the battery connected. $\therefore \Delta V_{\text{plate}} = V = \text{const}$

$$\downarrow C \propto \frac{1}{d} \uparrow$$

$$\therefore Q = C \cdot V$$

$$\therefore \downarrow Q \propto C \downarrow$$

$$Q_1 = C_1 \cdot V \leftarrow d_1 \rightarrow$$

$$C_1 = \frac{\epsilon A}{d_1} \rightarrow C_2 = \frac{\epsilon A}{d_2}$$

$$Q_2 = C_2 \cdot V$$

$$\text{initial charge on the plates } (Q_1) = C_1 \cdot V = \frac{\epsilon A \cdot V}{d_1}$$

$$\text{final " " " } (Q_2) = C_2 \cdot V = \frac{\epsilon A \cdot V}{d_2}$$

Diff. of charge on P_1

$$\Delta Q = (Q_2 - Q_1) = \epsilon A V \cdot \left\{ \frac{1}{d_2} - \frac{1}{d_1} \right\}$$

$$\Rightarrow \Delta Q = \frac{\epsilon A V (d_1 - d_2)}{d_1 d_2} = -ve$$

ii) work done in this process by the battery

$$W_{\text{Batt}} = \Delta Q \times \Delta V_{\text{Batt}} = \frac{\epsilon A \cdot V^2 (d_1 - d_2)}{d_1 d_2} = -ve$$

iii) initial charge on the plates $(Q) = C_1 \cdot V = \frac{\epsilon A \cdot V}{d_1} = \text{const}$

as we remove the Batt. charge becomes const.

$$W_{\text{ext}} = \Delta U = U_f - U_i = \frac{1}{2} \cdot \frac{Q^2}{C_2} - \frac{1}{2} \frac{Q^2}{C_1}$$


$$W_{ext} = \Delta U = U_f - U_i = \frac{1}{2} \cdot \frac{q^2}{C_2} - \frac{1}{2} \frac{q^2}{C_1}$$

$$= \frac{\epsilon^2 A^2 V^2}{2 d_1^2} \cdot \left\{ \frac{d_2}{\epsilon A} - \frac{d_1}{\epsilon A} \right\}$$

$$W_{ext} = \frac{\epsilon A \cdot V^2}{2 d_1^2} \cdot (d_2 - d_1) = +ve$$

Q: Two capacitors $C_1 = 4 \mu F$ & $C_2 = 2 \mu F$ are charged upto same p.d $V = 500$ volt then connected together as shown find.

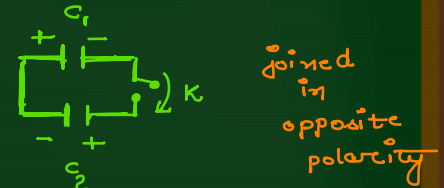- common potential on each capacitor
- final charge on each capacitor
- charge flow through the key
- Heat lost in surroundings



Sol: \rightarrow i) common potential (V) = $\frac{C_1 V_1 - C_2 V_2}{C_1 + C_2} = \frac{(2000 - 1000) \times 10^{-6}}{6 \times 10^{-6}} = \frac{1000}{6} = \frac{500}{3}$ volt

ii) final charge on C_1 (q_1') = $C_1 \cdot V = \frac{2000}{3} \mu C$

" " " C_2 (q_2') = $C_2 \cdot V = \frac{1000}{3} \mu C$

iii) charge flow through the key (Δq_1) = $|q_1 - q_1'| = \left(2000 - \frac{2000}{3}\right) \times 10^{-6}$
 $\Delta q_{key} = \frac{4000}{3} \times 10^{-6} C$

iv) heat lost (H) = $\frac{C_1 C_2 \cdot (V_1 + V_2)^2}{2(C_1 + C_2)} = \frac{8 \times 10^{-12} \times 10^6}{2 \times 6 \times 10^{-6}} = \frac{2}{3} J$

Q) calculate the heat lost after the switch is closed. Plate area is A & gap b/w the plates is d .

as $q_1 = q_4 = \frac{2Q + Q}{2} = \frac{3Q}{2}$

Let q charge flows from P_1 to P_2

P.D. b/w the plates

$$\Delta V = E \cdot d$$

$$0 = \vec{E}_1 + \vec{E}_2 + \vec{E}_3 + \vec{E}_4$$


as; $\vec{E}_1 = -\vec{E}_4$

$\therefore \vec{E}_2 = \vec{E}_3 = \frac{(Q - q)}{2 \epsilon_0 A}$

so $0 = 2 \cdot \frac{(Q - q)}{2 \epsilon_0 A} \Rightarrow \frac{Q}{2} = q$

so $q = \frac{Q}{2}$ — (2)

charge transferred after key is closed.

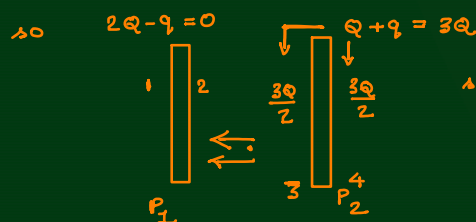

so $E = E_1 + E_2 + E_3 + E_4$
 $= 0 + 0 + \frac{q_3}{2 \epsilon_0 A} + \frac{q_4}{2 \epsilon_0 A}$
 $\Rightarrow E = \frac{3Q}{2 \epsilon_0 A}$ — (3)

so $U_i = \frac{1}{2} C \cdot \Delta V_i^2 = \frac{q}{8} \cdot \frac{\epsilon_0 A \times \frac{Q^2 \cdot d^2}{\epsilon^2 A^2}}{\epsilon^2 A^2}$ $\therefore \Delta V_i = E \cdot d = \frac{3Qd}{2 \epsilon_0 A}$ — (4)

$\therefore U_i = \frac{q Q^2 \cdot d}{8 \epsilon_0 A}$ — (5)

$$\therefore U_2 = \frac{q}{8} \frac{Q^2 \cdot d}{\epsilon A} \text{ --- (5)}$$

$$\text{so } W = |\Delta U| = |U_f - U_i| = \frac{q \cdot Q^2 \cdot d}{8 \epsilon A} = \frac{q Q^2}{8 C}$$

heat liberated. J