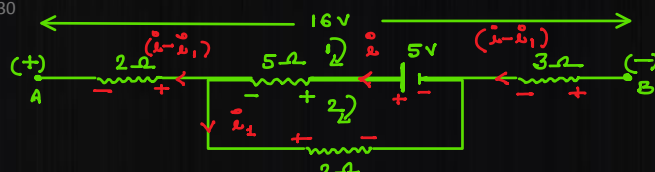


# Electric Current DPP-2 Level 1 Solutions

01 August 2020

00:30

Q1: →



KVL in loop 1

$$-2(i_2 - i_1) - 16 - 3(i_2 - i_1) + 5 - 5i_2 = 0$$

$$\Rightarrow 5i_1 - 10i_2 = 11 \quad \text{--- (1)}$$

KVL in loop 2

$$5i_2 - 5 + 2i_1 = 0$$

$$\Rightarrow 5i_2 + 2i_1 = 5 \quad \text{--- (2)}$$

eqn (2)  $\times 5$  - eqn (1)  $\times 2$

$$25i_2 + 10i_1 = 25$$


$$-10i_2 - 20i_1 = 22$$

$$45i_2 = 3$$

$$\therefore i_2 = \frac{1}{15} \text{ A (current flows through 5V battery)}$$

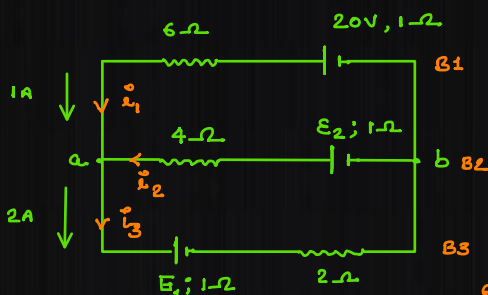Q2: →

all the 3 branches are in parallel combination about a & b.




at junction a: → from KCL

$$i_1 + i_2 = i_3$$

$$1 + i_2 = 2$$

$$i_2 = 1 \text{ A} \quad \text{--- (1)}$$

considering branch 1: →

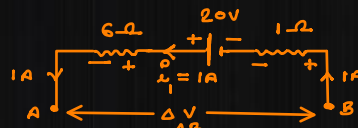

$$\Delta V_{AB} = -i_1 \times 1 + 20 - i_1 \times 6$$

$$= 20 - 7i_1$$

$$\text{as } i_1 = 1 \text{ A}$$


$$= 20 - 7 \times 1$$

potential diff.

$$\Delta V_{AB} = 13 \text{ volts} \quad \text{--- (2)}$$

b/w points a & b.

for branch 2: →

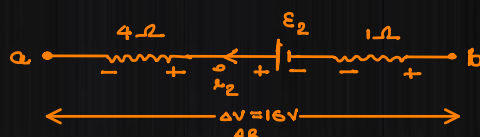



$$\text{here, } \Delta V_{AB} = -i_2 \times 1 + E_2 - 4i_2$$

$$13 = E_2 - 5 \times 1 \quad (\text{from eqn (1) \& (2)})$$

$$E_2 = 18 \text{ V} \quad \text{--- (3)}$$

for branch 3: →

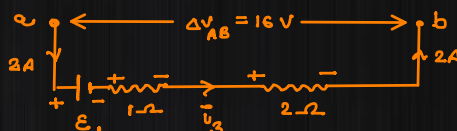

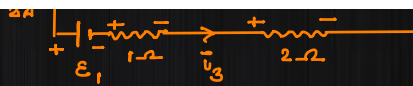


$$\Delta V_{AB} = 2 \cdot i_3 + 1 \cdot i_3 + \varepsilon_1$$

$$13 = 2 \times 2 + 1 \times 2 + \varepsilon_1$$

$$\therefore \varepsilon_1 = 13 - 6$$

$$\Rightarrow \varepsilon_1 = 7 \text{ volt} \quad \text{--- (4)}$$

Q3 :->

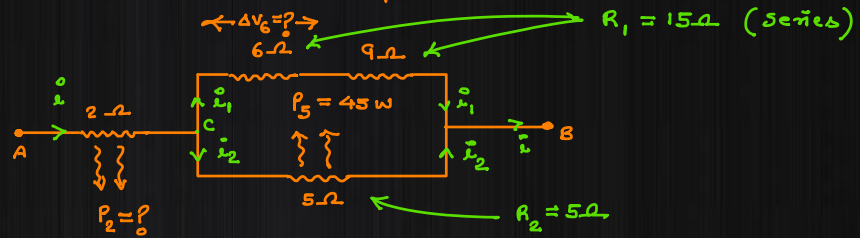

as power appeared 5 Ω resistor ( $P$ ) =  $\frac{V_1^2}{R}$

$$45 = \frac{V_1^2}{5}$$

$$V_1^2 = 9$$

$$\therefore V_1 = 3 \text{ A} \quad \text{--- (1)}$$

at junction :->

$$\frac{V_1}{V_2} = \frac{R_2}{R_1}$$

$$\frac{V_1}{3} = \frac{5}{15}$$

$$\therefore V_1 = 1 \text{ A} \quad \text{--- (2)}$$

so P.D. across 6 Ω resistor ( $\Delta V_{6\Omega}$ ) =  $V_1 \times R_6 = 1 \times 6 = 6 \text{ volt}$

as :  $V = V_1 + V_2$

$$\Rightarrow V = 4 \text{ A}$$


so power appeared across 2 Ω resistor

$$P_2 = \frac{V^2}{R}$$


$$= (4)^2 \times 2$$

$$P_2 = 32 \text{ W}$$

Q4) i)

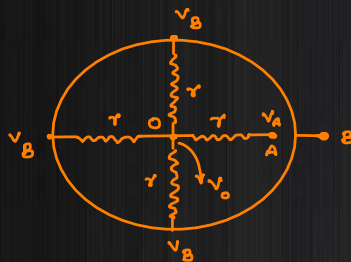

$\Rightarrow$

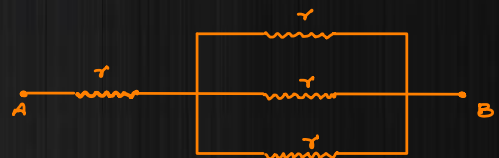

$\Downarrow$




$$\therefore R_{eq} = r + \frac{r}{3} = \frac{4r}{3}$$

ii)



$\Rightarrow$


Balanced wheat  
Stone Bridge

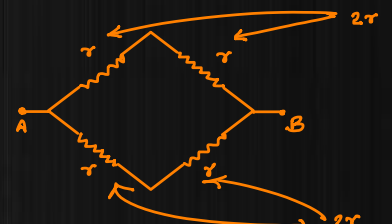

$$\therefore R_{eq} = \frac{2r}{2} = r$$

iii)

iii)

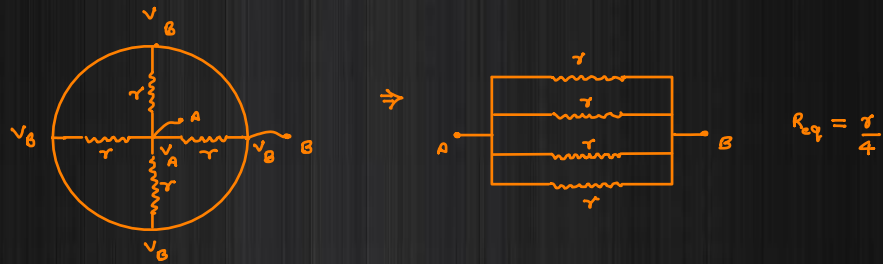

q5)

Let the Heat required to boil the water is  $H$  Joules.

If the Resistance of both the coils are  $R_1$  &  $R_2$ .

$$H = \frac{V^2}{R_1} \times t_1 = \frac{V^2}{R_2} \times t_2 \quad \text{--- (1)}$$

$$\therefore \frac{R_1}{R_2} = \frac{t_1}{t_2} = \frac{6}{8}$$

$$\therefore \frac{R_1}{R_2} = \frac{3}{4} \quad \text{--- (2)}$$

note: voltage of the power source is  $V$  in all the cases.

i) when connected in series;

$$H = \frac{V^2}{R_{eq}} \times t_s$$

$$\Rightarrow H = \frac{V^2}{R_1 + R_2} \times t_s$$

$$\Rightarrow H = \frac{V^2 \times t_s}{R_2 \cdot \left(\frac{R_1}{R_2} + 1\right)}$$

from (1);

$$\Rightarrow H = \frac{H \times t_s}{t_2 \left(\frac{3}{4} + 1\right)} \quad \{\because t_2 = 8 \text{ min}\}$$

$$\Rightarrow 8 \cdot \left\{\frac{3}{4} + 1\right\} = t_s$$

$$t_s = 14 \text{ min}$$

ii) when connected in parallel: →

$$H = \frac{V^2}{R_{eq}} \times t_p$$

$$= \frac{V^2 \cdot (R_1 + R_2)}{R_1 R_2} \cdot t_p$$

$$\Rightarrow H = \frac{V^2}{R_1} \cdot \left\{\frac{R_1}{R_2} + 1\right\} \cdot t_p$$

from eqn (1);

$$H = \frac{H}{t_1} \cdot \left\{\frac{3}{4} + 1\right\} \cdot t_p$$

$$\therefore t_1 = 6 \text{ min}$$

$$6 = \frac{t_p}{4}$$

$$\therefore t_p = \frac{24}{7} \text{ min} = 3 \text{ min } 42.85 \text{ sec.}$$

q6: → in next chapter


q7: →



as  $100\Omega$  &  $100\Omega$  are in parallel

$$\therefore \Delta V_{CD} = 100 \text{ volts}$$
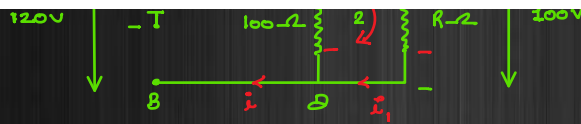
$$\therefore \Delta V_{CD} = i_2 \times 100$$



$$\begin{aligned}\therefore \Delta V_{CD} &= i_2 \times 100 \\ 100 &= i_2 \times 100 \\ i_2 &= 1 \text{ A} \quad \text{--- (1)}\end{aligned}$$

KVL in loop ①

$$-10i_1 - 100i_2 + 120 = 0$$

$$\Rightarrow 10i_1 = 120 - 100$$

$$\Rightarrow i_1 = \frac{20}{10}$$

$$\therefore i_1 = 2 \text{ A} \quad \text{--- (2)}$$

$$\therefore i = i_1 + i_2$$

$$2 = i_1 + 1$$

$$\Rightarrow i_1 = 1 \text{ Amp} \quad \text{--- (3)}$$


$$\therefore \Delta V_R = i_1 \times R$$

$$\Rightarrow 100 = 1 \times R$$

$$\therefore R = 100 \Omega$$

Q8: in next chapter:

Q9:

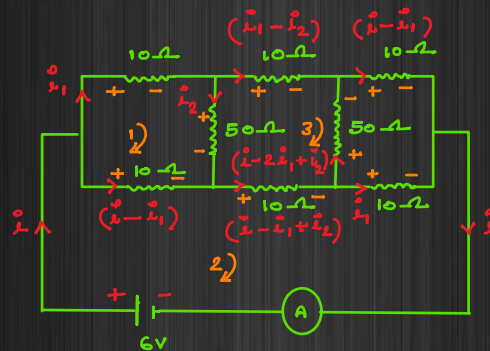

it is a mirror symmetry problem

KVL in loop ①

$$-10i_1 - 50i_2 + 10(i - i_1) = 0$$

$$\Rightarrow 10i - 20i_1 - 50i_2 = 0$$

$$\Rightarrow i - 2i_1 - 5i_2 = 0 \quad \text{--- (1)}$$

KVL in loop 2

$$-10(i_1 - i_2) + 50(i - 2i_1 + i_2) + 10(i - i_1 + i_2) + 50i_2 = 0$$

$$\Rightarrow -120i_1 + 120i_2 + 60i = 0$$

$$\Rightarrow i + 2i_2 - 2i_1 = 0 \quad \text{--- (2)}$$

KVL in loop ②:  $\rightarrow$

$$-10(i - i_1) - 10(i - i_1 + i_2) - 10i_1 + 6 = 0$$

$$\Rightarrow -20i + 10i_1 - 10i_2 + 6 = 0$$

$$\Rightarrow -10i + 5i_1 - 5i_2 + 3 = 0 \quad \text{--- (3)}$$

eqn ① - eqn ②

$$-7i_2 = 0$$

$$\therefore i_2 = 0 \quad \text{--- (4)}$$

from ② & ④

$$i - 2i_1 = 0$$

$$\therefore i_1 = \frac{i}{2} \quad \text{--- (5)}$$

from ③ & ④ & ⑤

$$-10i + \frac{5i}{2} - 0 + 3 = 0$$

$$3 = \frac{15i}{2}$$

$$\therefore i = \frac{2}{3} = 0.4 \text{ A} ; \text{ Reading of the}$$

$$3 = \frac{15 \times \frac{1}{2}}{2}$$

$$\therefore I = \frac{2}{5} = 0.4 \text{ A} ; \text{Reading of the } \textcircled{A}$$

Q.10)



$$\therefore V = A \times l = \text{const.}$$

$$\text{so } A = \frac{V}{l} \text{ --- (2)}$$

$$\therefore R = \frac{\rho \cdot l}{A} \text{ --- (1)}$$

$$\text{from (1) \& (2)}$$

$$R = \frac{\rho \cdot l^2}{V}$$

$$\therefore \rho \& V \text{ are const.}$$

$$\therefore \frac{\Delta R}{R} \times 100\% = 2 \cdot \frac{\Delta l}{l} \times 100\%$$

$$= 2 \times 0.1\%$$

$$\Rightarrow \frac{\Delta R}{R} \times 100\% = 0.2\%, \text{ increase}$$

Q.11)

power supplied to or consumed by the load ( $P$ ) =  $V \times I$

$$\therefore I = \frac{P}{V} \text{ --- (1)} ; \text{current in the cables}$$

$$\text{so power loss in cables } (\Delta P) = I^2 \cdot R$$

$$\Rightarrow \Delta P = \frac{P^2}{V^2} \times R \text{ --- (2)}$$

a) if  $V = 10^4 \text{ volts}$  &  $P = 10^5 \text{ W}$

$$\Delta P = \frac{10^5}{10^8} \times 5$$

$$\therefore \Delta P = 500 \text{ W}$$

b) if  $V = 2 \times 10^5 \text{ volts}$  &  $P = 10^5 \text{ W}$

$$\Delta P = 1.25 \text{ W}$$

Q.12)  $\Rightarrow$  when the switch  $S_0$  is open  $\Rightarrow$  cell is open circuit



so  $V_{AB} = E = \text{reading of the voltmeter when } S_0 \text{ is open}$

$$\therefore E = 1.52 \text{ volt --- (1)}$$

when the  $S_0$  is closed; P.D. across the points A & B


$$V = E - Ir$$


new reading of the voltmeter  $\Rightarrow 1.45 = 1.52 - 1 \times r$

Reading of the Ammeter  $\therefore r = 1.52 - 1.45$

$$\Rightarrow r = 0.07 \Omega$$

Q.13)

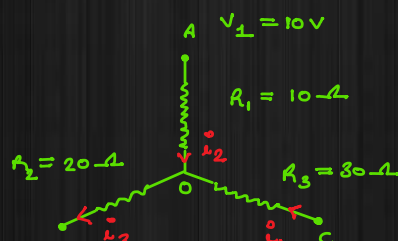

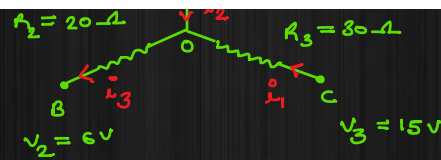

at node O : from KVL

$$i_1 + i_2 = i_3$$

$$\Rightarrow \left( \frac{V_0 - V_2}{R_1} \right) + \left( \frac{V_0 - V_3}{R_2} \right) = \left( \frac{V_0 - V_D}{R_3} \right)$$

$$\Rightarrow \left( \frac{15 - V_0}{30} \right) + \left( \frac{10 - V_0}{20} \right) = \left( \frac{V_0 - 6}{30} \right)$$

$$\Rightarrow 30 - 2V_0 + 60 - 6V_0 = 3V_0 - 18$$

$$\Rightarrow 11V_0 = 108$$

$$\text{potential at the node } V_0 = \frac{108}{11} \text{ volt}$$

$$\therefore i_1 = \frac{V_0 - V_2}{R_1} = \frac{15 - \frac{108}{11}}{30} = \frac{57}{330} = \frac{19}{110} \text{ A}$$

$$i_2 = \frac{V_0 - V_3}{R_2} = \frac{10 - \frac{108}{11}}{20} = \frac{2}{110} = \frac{1}{55} \text{ A}$$

$$i_3 = \frac{V_0 - V_D}{R_3} = \frac{\frac{108}{11} - 6}{30} = \frac{42}{220} = \frac{21}{110} \text{ A}$$

Q14)

$\therefore$  Distribution of electric current among resistances in parallel combination always takes place in inverse ratio of resistance.

$$\begin{aligned} \therefore i_1 : i_2 : i_3 &= R_3 : R_2 : R_1 \\ &= \frac{l_1^2}{A_3} : \frac{l_2^2}{A_2} : \frac{l_3^2}{A_1} \\ &= \frac{l_1^2}{r_3^2} : \frac{l_2^2}{r_2^2} : \frac{l_3^2}{r_1^2} \\ &= \frac{4}{25} : \frac{3}{16} : \frac{2}{9} \end{aligned}$$

Here  $A = \pi r^2$


$$\Rightarrow i_1 : i_2 : i_3 = 54 : 64 : 75$$

Q15)

$$\therefore P = \frac{V^2}{R}$$

$$\therefore \text{resistance of } B_1 (R_1) = \frac{V^2}{P_1}$$

$$B_2 (R_2) = \frac{V^2}{P_2}$$

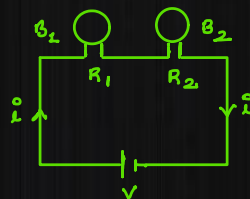

$$\text{current in the circuit } (i) = \frac{V}{R_{eq}} = \frac{V}{(R_1 + R_2)}$$

$\therefore$  Total Power consumption

$\therefore$  Total Power consumption

$$P = I^2 \cdot R_{eq}$$

$$= \frac{V^2}{(R_1 + R_2)^2} \times (R_1 + R_2)$$

$$= \frac{V^2}{(R_1 + R_2)}$$

$$= \frac{V^2}{\frac{V^2}{P_1} + \frac{V^2}{P_2}}$$

$$\therefore P = \frac{P_1 \cdot P_2}{P_1 + P_2} \text{ watt}$$